

ITP

PSpice®

Simulation of Power Electronics Circuits

An introductory guide

R. Ramshaw and D. Schuurman

2-006-32-1



CHAPMAN & HALL

CONTENTS

Preface	IX
Chapter 1 PSpice and Electric Circuits	1
1.1 INTRODUCTION	1
1.2 PSPICE	2
1.3 CIRCUIT DESCRIPTION FOR PSPICE SIMULATION	4
1.3.1 DC Analysis (DC Source)	4
1.3.2 Transient Analysis (AC Source)	16
1.3.3 Transient Analysis (PWL Source)	24
1.4 OPERATIONAL AMPLIFIERS	30
1.4.1 The Ideal Op-amp	30
1.4.2 Built-in Op-amp Macro Model	35
1.4.3 A Comparator	38
1.4.4 Built-in Comparator Macro Model	44
Chapter 2 PSpice Switches and Power Modulation	45
2.1 INTRODUCTION	45
2.2 DC-DC MODULATION SIMULATION	45
2.2.1 Chopper Switch	46
2.3 DC-AC MODULATION SIMULATION	54
2.3.1 Inverter Switches and Subcircuits	55
Chapter 3 Waveform Distortion	70
3.1 INTRODUCTION	70
3.2 AVERAGE VALUES	70
3.3 RMS VALUES	75
3.4 POWER AND ENERGY	81
3.5 HARMONICS	85
Chapter 4 Ideal Semiconductor Switches	95
4.1 INTRODUCTION	95
4.2 THE IDEAL DIODE	96
4.2.1 Voltage-controlled Switch as the Diode	97

4.2.2	Current-controlled Switch as the Diode	103
4.2.3	VCCS as the Diode	105
4.2.4	PSpice Rectifier, the Diode	109
4.3	THE IDEAL BJT TRANSISTOR AS A SWITCH	112
4.3.1	Ideal BJT Chopper	113
4.4	THE IDEAL THYRISTOR	116
4.4.1	Ideal Thyristor Rectifier	117
4.5	THE IDEAL TRIAC	122
4.5.1	Ideal-triac Voltage Regulator	123
4.6	THE IDEAL GTO	127
4.6.1	Chopper Circuit Ideal GTO	129
4.7	THE IDEAL MOSFET AND IGBT SWITCHES	133
4.7.1	Chopper (Ideal MOSFET or IGBT)	134
4.8	THE IDEAL MCT	137
4.8.1	Chopper (Ideal MCT)	138
Chapter 5 Simulation of Driver Circuits		143
5.1	INTRODUCTION	143
5.2	DRIVERS FOR DC-DC CONVERSION	143
5.2.1	Chopper Duty-cycle Control	148
5.3	DRIVERS FOR AC-DC CONVERSION	158
5.3.1	Single-phase Half-wave Conversion	158
5.4	DRIVERS FOR DC-AC CONVERSION	164
5.4.1	Introduction	164
5.4.2	A Single-pulse Driver	164
5.4.3	A Uniform Multiple-pulse Driver	169
5.4.4	A Modulating PWM Driver (SPWM)	171
Chapter 6 DC-DC Converter Circuits		176
6.1	INTRODUCTION	176
6.2	THE BUCK CONVERTER	176
6.3	THE BOOST CONVERTER	182
6.4	THE BUCK-BOOST CONVERTER	186
6.5	THE FLYBACK CONVERTER (TRANSFORMER)	189
Chapter 7 Diode Rectifiers		194
7.1	INTRODUCTION	194
7.2	SINGLE-PHASE HALF-WAVE RECTIFICATION	194
7.3	SINGLE-PHASE FULL-WAVE RECTIFICATION	197

7.4	BIPHASE RECTIFICATION	198
7.4.1	Transformer Model	198
7.5	THREE-PHASE HALF-WAVE RECTIFICATION	208
7.5.1	Simulation Convergence	210
7.6	THREE-PHASE FULL-WAVE RECTIFICATION	215
Chapter 8 Controlled Rectification		220
8.1	INTRODUCTION	220
8.2	SINGLE-PHASE HALF-WAVE CONTROLLED RECTIFICATION	220
8.3	SINGLE-PHASE FULL-WAVE CONTROLLED RECTIFICATION	224
8.4	BIPHASE CONTROLLED RECTIFICATION	228
8.5	THREE-PHASE HALF-WAVE CONTROLLED RECTIFICATION	229
8.6	HALF-CONTROLLED THREE-PHASE BRIDGE RECTIFICATION	230
8.7	THREE-PHASE FULLY-CONTROLLED RECTIFICATION	231
Chapter 9 Switch-mode Inverters		239
9.1	INTRODUCTION	239
9.2	CENTRE-TAPPED SOURCE INVERTER	239
9.2.1	Uniform Multiple-pulse Inverter	245
9.2.2	SPWM Inverter	246
9.2.3	SPWM Inverter Digital Driver	247
9.2.4	Current-regulated Inverter	247
9.3	SINGLE-PHASE BRIDGE INVERTER	255
9.3.1	Uniform Multiple-pulse Inverter	260
9.3.2	Sinewave Pulse-width Modulation SPWM	265
9.3.3	Current-source Inverter	271
9.3.4	Cycloconverter	271
9.4	THREE-PHASE SWITCH-MODE INVERTERS	271
9.4.1	Six-step Mode Inverter	271
9.4.2	Sinewave Pulse-width Modulation SPWM	276

Chapter 10 Resonant Converters	283
10.1 INTRODUCTION	283
10.2 RESONANT-LOAD INVERTERS	283
10.2.1 Series-load Resonant Inverter	284
10.2.2 Parallel-load Resonant Inverter	288
10.3 RESONANT-SWITCH CONVERTERS	292
10.3.1 Zero-current Switching Converters	292
10.3.2 Zero-voltage Switching Converters	300
10.4 INTEGRAL-CYCLE CONVERTERS	304
Chapter 11 Advanced Topics	305
11.1 INTRODUCTION	305
11.2 THE JUNCTION DIODE MODEL	306
11.2.1 Library Models of the Junction Diode	308
11.2.2 A Diode's Model Parameters	311
11.2.3 Model Parameters and PARTS	318
11.3 THE THYRISTOR	322
11.4 THE TRIAC	326
11.5 THE MOSFET AND PERFORMANCE ANALYSIS	329
11.6 THE BJT AND PERFORMANCE OPTIMIZATION	337
11.7 THE IGBT, GTO AND MCT	344
Appendix A Library Files	345
Appendix B List of Circuit-file Examples	347
Appendix C Quick Reference to PSpice Statements	350
Appendix D Bibliography	358
Appendix E WEBSITE	360
Appendix F Problems	362
Index	382