

3RD EDITION

# NETWORK ANALYSIS

M. E. VAN VALKENBURG

# Contents

	<b>PREFACE TO THE THIRD EDITION</b>	<b>xi</b>
	<b>PREFACE TO THE SECOND EDITION</b>	<b>xiii</b>
<b>1</b>	<b>DEVELOPMENT OF THE CIRCUIT CONCEPT</b>	<b>1</b>
	1-1 Introduction 1	
	1-2 Charge and Energy 2	
	1-3 The Relationship of Field and Circuit Concepts 6	
	1-4 The Capacitance Parameter 6	
	1-5 The Inductance Parameter 10	
	1-6 The Resistance Parameter 16	
	1-7 Units and Scaling 19	
	1-8 Approximation of a Physical System as a Circuit 20	
<b>2</b>	<b>CONVENTIONS FOR DESCRIBING NETWORKS</b>	<b>34</b>
	2-1 Reference Directions for Current and Voltage 34	
	2-2 Active Element Conventions 36	
	2-3 The Dot Convention for Coupled Circuits 38	
	2-4 Topological Description of Networks 42	
<b>3</b>	<b>NETWORK EQUATIONS</b>	<b>50</b>
	3-1 Kirchhoff's Laws 50	
	3-2 The Number of Network Equations 53	

3-3	<i>Source Transformations</i>	57	
3-4	<i>Examples of the Formulation of Network Equations</i>	61	
3-5	<i>Loop Variable Analysis</i>	67	
3-6	<i>Node Variable Analysis</i>	73	
3-7	<i>Determinants: Minors and the Gauss Method</i>	76	
3-8	<i>Duality</i>	81	
3-9	<i>State Variable Analysis</i>	83	
<b>4</b>	<b>FIRST-ORDER DIFFERENTIAL EQUATIONS</b>		<b>99</b>
4-1	<i>General and Particular Solutions</i>	99	
4-2	<i>Time Constants</i>	103	
4-3	<i>The Integrating Factor</i>	106	
4-4	<i>More Complicated Networks</i>	109	
<b>5</b>	<b>INITIAL CONDITIONS IN NETWORKS</b>		<b>118</b>
5-1	<i>Why Study Initial Conditions?</i>	118	
5-2	<i>Initial Conditions in Elements</i>	119	
5-3	<i>Geometrical Interpretation of Derivatives</i>	123	
5-4	<i>A Procedure for Evaluating Initial Conditions</i>	125	
5-5	<i>Initial State of a Network</i>	129	
<b>6</b>	<b>DIFFERENTIAL EQUATIONS, CONTINUED</b>		<b>139</b>
6-1	<i>Second-order Equation; Internal Excitation</i>	139	
6-2	<i>Higher-order Equations; Internal Excitation</i>	147	
6-3	<i>Networks Excited by External Energy Sources</i>	148	
6-4	<i>Response as Related to the s-Plane Location of Roots</i>	154	
6-5	<i>General Solutions in Terms of S, Q, and <math>\omega_n</math></i>	158	
<b>7</b>	<b>THE LAPLACE TRANSFORMATION</b>		<b>170</b>
7-1	<i>Introduction</i>	170	
7-2	<i>The Laplace Transformation</i>	172	
7-3	<i>Some Basic Theorems for the Laplace Transformation</i>	176	
7-4	<i>Examples of the Solution of Problems with the Laplace Transformation</i>	179	
7-5	<i>Partial Fraction Expansion</i>	181	
7-6	<i>Heaviside's Expansion Theorem</i>	186	
7-7	<i>Examples of Solution by the Laplace Transformation</i>	189	
<b>8</b>	<b>TRANSFORMS OF OTHER SIGNAL WAVEFORMS</b>		<b>202</b>
8-1	<i>The Shifted Unit Step Function</i>	202	
8-2	<i>The Ramp and Impulse Functions</i>	207	

8-3	<i>Waveform Synthesis</i>	213	
8-4	<i>The Initial and Final Value of <math>f(t)</math> from <math>F(s)</math></i>	220	
8-5	<i>The Convolution Integral</i>	222	
8-6	<i>Convolution as a Summation</i>	230	
<b>9</b>	<b>IMPEDANCE FUNCTIONS AND NETWORK THEOREMS</b>		<b>242</b>
9-1	<i>The Concept of Complex Frequency</i>	242	
9-2	<i>Transform Impedance and Transform Circuits</i>	246	
9-3	<i>Series and Parallel Combinations of Elements</i>	250	
9-4	<i>Superposition and Reciprocity</i>	255	
9-5	<i>Thévenin's Theorem and Norton's Theorem</i>	259	
<b>10</b>	<b>NETWORK FUNCTIONS; POLES AND ZEROS</b>		<b>279</b>
10-1	<i>Terminal Pairs or Ports</i>	279	
10-2	<i>Network Functions for the One Port and Two Port</i>	280	
10-3	<i>The Calculation of Network Functions</i>	285	
	(1) <i>Ladder Networks</i>	285	
	(2) <i>General Networks</i>	288	
10-4	<i>Poles and Zeros of Network Functions</i>	290	
10-5	<i>Restrictions on Pole and Zero Locations for Driving-Point Functions</i>	293	
10-6	<i>Restrictions on Pole and Zero Locations for Transfer Functions</i>	298	
10-7	<i>Time-domain Behavior from the Pole and Zero Plot</i>	301	
10-8	<i>Stability of Active Networks</i>	307	
<b>11</b>	<b>TWO-PORT PARAMETERS</b>		<b>325</b>
11-1	<i>Relationship of Two-Port Variables</i>	325	
11-2	<i>Short-Circuit Admittance Parameters</i>	326	
11-3	<i>The Open-Circuit Impedance Parameters</i>	328	
11-4	<i>Transmission Parameters</i>	331	
11-5	<i>The Hybrid Parameters</i>	334	
11-6	<i>Relationships Between Parameter Sets</i>	336	
11-7	<i>Parallel Connection of Two-Port Networks</i>	338	
<b>12</b>	<b>SINUSOIDAL STEADY-STATE ANALYSIS</b>		<b>351</b>
12-1	<i>The Sinusoidal Steady State</i>	351	
12-2	<i>The Sinusoid and <math>e^{\pm j\omega t}</math></i>	353	
12-3	<i>Solution Using <math>e^{\pm j\omega t}</math></i>	355	
12-4	<i>Solution Using <math>\text{Re}^{j\omega t}</math> or <math>\text{Im} e^{j\omega t}</math></i>	358	
12-5	<i>Phasors and Phasor Diagrams</i>	360	

<b>13</b>	<b>FREQUENCY RESPONSE PLOTS</b>	<b>372</b>
	13-1 <i>Parts of Network Functions</i>	372
	13-2 <i>Magnitude and Phase Plots</i>	373
	13-3 <i>Complex Loci</i>	376
	13-4 <i>Plots from s-Plane Phasors</i>	379
	13-5 <i>Bode Diagrams</i>	387
	13-6 <i>The Nyquist Criterion</i>	395
<b>14</b>	<b>INPUT POWER, POWER TRANSFER, AND INSERTION LOSS</b>	<b>419</b>
	14-1 <i>Energy and Power</i>	420
	14-2 <i>Effective or Root-Mean-Square Values</i>	424
	14-3 <i>Average Power and Complex Power</i>	427
	14-4 <i>Problems in Optimizing Power Transfer</i>	430
	14-5 <i>Insertion Loss</i>	434
	14-6 <i>Tellegen's Theorem</i>	437
<b>15</b>	<b>FOURIER SERIES AND SIGNAL SPECTRA</b>	<b>452</b>
	15-1 <i>Fourier Series</i>	452
	15-2 <i>Evaluation of Fourier Coefficients</i>	455
	15-3 <i>Waveform Symmetries as Related to Fourier Coefficients</i>	460
	15-4 <i>Convergence in Truncated Series</i>	467
	15-5 <i>Exponential Form of the Fourier Series</i>	472
	15-6 <i>Steady-State Response to Periodic Signals</i>	477
<b>16</b>	<b>FOURIER INTEGRAL AND CONTINUOUS SPECTRA</b>	<b>490</b>
	16-1 <i>Spectrum Envelope for a Recurring Pulse</i>	490
	16-2 <i>The Fourier Integral and Transform</i>	493
	16-3 <i>Application in Network Analysis</i>	495
	16-4 <i>Some Useful Fourier Transforms</i>	499
	16-5 <i>The Relationship of Fourier and Laplace Transforms</i>	504
	16-6 <i>Bandwidth and Pulse Duration</i>	506
	16-7 <i>Bandwidth and Rise Time</i>	510
<b>APPENDICES</b>		
<b>A</b>	<b>ALGEBRA OF COMPLEX NUMBERS (PHASORS)</b>	<b>519</b>
	A-1 <i>Definitions</i>	519
	A-2 <i>Addition and Subtraction</i>	520
	A-3 <i>Multiplication</i>	521
	A-4 <i>Division</i>	522
	A-5 <i>Logarithm of a Complex Number</i>	523
	A-6 <i>Roots and Powers of Complex Numbers</i>	523

<b>B</b>	<b>MATRIX ALGEBRA</b>	<b>525</b>
	<i>B-1 Definitions</i>	525
	<i>B-2 Addition and Subtraction of Matrices</i>	526
	<i>B-3 Multiplication of Matrices</i>	526
	<i>B-4 Other Definitions</i>	527
	<i>B-5 Matrix Solution of Simultaneous Linear Equations</i>	528
<b>C</b>	<b>SCALING</b>	<b>532</b>
	<i>C-1 An Example of Scaling</i>	532
	<i>C-2 Frequency and Magnitude Scaling</i>	533
<b>D</b>	<b>TABLE OF INVERSE LAPLACE TRANSFORMS</b>	<b>537</b>
<b>E</b>	<b>DIGITAL COMPUTER EXERCISES</b>	<b>540</b>
	<i>E-1 Numerical Methods for Finding Roots</i>	540
	<i>E-2 Numerical Integration</i>	540
	<i>E-3 Matrix Formulation and Matrix Operations</i>	541
	<i>E-4 Solving Simultaneous Linear Algebraic Equations</i>	541
	<i>E-5 Algebraic Operations</i>	541
	<i>E-6 Solution of Ordinary Differential Equations</i>	541
	<i>E-7 Solution of Nonlinear Differential Equations</i>	542
	<i>E-8 Network Analysis</i>	542
	<i>E-9 Computer Determination of Magnitude and Phase Plotting</i>	542
	<i>E-10 References</i>	542
<b>F</b>	<b>REFERENCES</b>	<b>544</b>
	<i>F-1 Elementary or Intermediate Textbooks</i>	544
	<i>F-2 Advanced Textbooks on Circuit Theory</i>	547
	<i>F-3 Computer Oriented Circuit Theory Textbooks</i>	548
	<i>F-4 Device Modeling</i>	549
	<i>F-5 Systems</i>	550
	<i>F-6 Background Material or Material of Historical Interest</i>	550
<b>G</b>	<b>ANSWERS TO SELECTED PROBLEMS</b>	<b>552</b>
<b>H</b>	<b>HISTORICAL NOTES</b>	<b>559</b>