

JACOB MILLMAN

**MICRO-
ELECTRONICS**

Digital and Analog Circuits and Systems

CONTENTS

Preface

xii

Prologue: A Brief History of Electronics

xvii

Part 1 Semiconductor Device Characteristics

1	Semiconductors	1
1-1	Charged Particles	1
1-2	Field Intensity, Potential, Energy	2
1-3	The eV Unit of Energy	4
1-4	Mobility and Conductivity	5
1-5	Electrons and Holes in an Intrinsic Semiconductor	9
1-6	Donor and Acceptor Impurities	12
1-7	Charge Densities in a Semiconductor	14
1-8	Electrical Properties of Ge and Si	15
1-9	The Hall Effect	17
1-10	Thermistors and Sensitors	19
1-11	Diffusion	19
1-12	The Potential Variation within a Graded Semiconductor	21
1-13	Recapitulation	23
	References	24
	Review Questions	24
2	Junction-Diode Characteristics	26
2-1	The Open-Circuited p - n Junction	26
2-2	The p - n Junction as a Rectifier	29
2-3	The Volt-Ampere Characteristic	32
2-4	The Temperature Dependence of the V/I Characteristic	35
2-5	Diode Resistance	36
2-6	Space-Charge, or Transition, Capacitance C_T	37
2-7	Minority-Carrier Storage in a Diode	41
2-8	Diffusion Capacitance	44
2-9	Breakdown Diodes	45
2-10	The Diode as a Circuit Element	48
2-11	The Load-Line Concept	49
2-12	The Piecewise Linear Diode Model	50

2-13	Junction-Diode Switching Times	52
	References	54
	Review Questions	55
3	Bipolar Transistor Characteristics	57
3-1	The Junction Transistor	57
3-2	Transistor Current Components	60
3-3	The Transistor as an Amplifier	62
3-4	Transistor Construction	63
3-5	The Common-Base (CB) Configuration	65
3-6	The Common-Emitter (CE) Configuration	68
3-7	The CE Cutoff Currents	73
3-8	The CE Saturation Region	74
3-9	Typical Transistor—Junction Voltage Values	77
3-10	Common-Emitter Current Gain	80
3-11	Inverted Mode of Operation	81
3-12	Transistor Ratings	82
3-13	Additional Transistor Characteristics	85
3-14	Transistor Switching Times	85
	References	88
	Review Questions	88
4	Integrated Circuits: Fabrication and Characteristics	91
4-1	Integrated-Circuit (Microelectronic) Technology	91
4-2	Basic Monolithic Integrated Circuits	93
4-3	Epitaxial Growth	98
4-4	Masking and Etching	98
4-5	Diffusion of Impurities	100
4-6	Transistors for Monolithic Circuits	101
4-7	Monolithic Diodes	105
4-8	The Metal-Semiconductor Contact	107
4-9	Integrated Resistors	109
4-10	Integrated Capacitors	113
4-11	Characteristics of Integrated Components	114
4-12	Monolithic-Circuit Layout	115
4-13	Additional Isolation Methods	118
	References	119
	Review Questions	119

Part 2 Digital Circuits and Systems

5	Digital Circuits	123
5-1	Digital (Binary) Operation of a System	123
5-2	The OR Gate	125
5-3	The AND Gate	128

5-4	The NOT (INVERTER) Circuit	130
5-5	The INHIBIT (ENABLE) Operation	132
5-6	The EXCLUSIVE-OR Circuit	133
5-7	De Morgan's Laws	135
5-8	The NAND and NOR Diode-Transistor Logic (DTL) Gates	137
5-9	Modified (Integrated-Circuit) DTL Gates	140
5-10	High-Threshold-Logic (HTL) Gate	145
5-11	Transistor-Transistor-Logic (TTL) Gate	146
5-12	Output Stages	148
5-13	Resistor-Transistor Logic (RTL) and Direct-Coupled Transistor Logic (DCTL)	152
5-14	Emitter-Coupled Logic (ECL)	155
5-15	Comparison of Logic Families	160
	References	163
	Review Questions	164
6	Combinational Digital Systems	166
6-1	Standard Gate Assemblies	166
6-2	Binary Adders	169
6-3	Arithmetic Functions	175
6-4	Digital Comparator	177
6-5	Parity Checker/Generator	180
6-6	Decoder/Demultiplexer	181
6-7	Data Selector/Multiplexer	186
6-8	Encoder	189
6-9	Read-Only Memory (ROM)	193
6-10	Two-dimensional Addressing of a ROM	197
6-11	ROM Applications	199
	References	202
	Review Questions	203
7	Sequential Digital Systems	205
7-1	A 1-Bit Memory	205
7-2	The Clocked <i>S-R</i> FLIP-FLOP	208
7-3	<i>J-K</i> , <i>T</i> , and <i>D</i> -Type FLIP-FLOPS	210
7-4	Shift Registers	215
7-5	Ripple (Asynchronous) Counters	220
7-6	Synchronous Counters	225
7-7	Applications of Counters	228
	References	231
	Review Questions	231
8	Field-Effect Transistors	234
8-1	The Junction Field-Effect Transistor	235
8-2	The JFET Volt-Ampere Characteristics	237
8-3	Fabrication of JFETs	241
8-4	The Enhancement Metal-Oxide-Semiconductor Field-Effect Transistor (MOSFET)	242

8-5	The Depletion MOSFET	247
8-6	Technological Improvements	249
8-7	MOSFET Inverters	253
8-8	MOSFET Logic Gates	259
8-9	Complementary MOSFETs	263
	References	267
	Review Questions	267
9	Large-Scale Integration Systems	269
9-1	Dynamic MOS Shift Registers	269
9-2	Ratioless Shift-Register Stages	273
9-3	MOS Read-Only Memory	276
9-4	Erasable-Programmable Read-Only Memory (EPROM)	279
9-5	Programmable Logic Array (PLA)	283
9-6	Random-Access Memory (RAM)	286
9-7	Read/Write Memory Cells	291
9-8	Charge-Coupled Device (CCD)	298
9-9	CCD Structures	302
9-10	CCD Memory Organizations	308
9-11	Microprocessor and Microcomputer	312
9-12	Integrated-Injection Logic (I ² L)	315
9-13	Injection Logic Circuits	321
	References	325
	Review Questions	326

Part 3 Analog Circuits and Systems

10	Analog Diode Circuits	333
10-1	A Simple Application	333
10-2	Clipping (Limiting) Circuits	335
10-3	Clipping at Two Independent Levels	338
10-4	A Breakdown-Diode Voltage Regulator	342
10-5	Rectifiers	343
10-6	Other Full-Wave Circuits	348
10-7	Capacitor Filters	350
10-8	Additional Diode Circuits	354
	Reference	356
	Review Questions	356
11	Low-Frequency Amplifiers	358
11-1	The Operating Point of a BJT	359
11-2	Bias Stability	361
11-3	Self-Bias or Emitter Bias	363
11-4	Stabilization against Variations in I_{CO} , V_{BE} , and β	365
11-5	Output Waveforms for a Sinusoidal Input	370
11-6	Approximate Small-Signal BJT Models	372
11-7	The Transistor Transconductance	373

11-8	Linear Analysis of a Transistor Circuit	375
11-9	The Common-Emitter (CE) Amplifier	376
11-10	The Emitter Follower	379
11-11	The Common-Base (CB) Amplifier	381
11-12	Comparison of BJT Amplifier Configurations	381
11-13	The CE Amplifier with an Emitter Resistor	382
11-14	Cascading Transistor Amplifiers	384
11-15	Accurate Small-Signal BJT Models	389
11-16	High-Input-Resistance BJT Circuits	393
11-17	Biasing the Field-Effect Transistor	397
11-18	The JFET or MOSFET Small-Signal Model	400
11-19	The Low-Frequency Common-Source and Common-Drain Amplifiers	402
11-20	The JFET as a Voltage-Controlled Resistor (VCR)	405
	References	406
	Review Questions	406
12	Feedback Amplifier Characteristics	409
12-1	Classification of Amplifiers	409
12-2	The Feedback Concept	411
12-3	The Transfer Gain with Feedback	414
12-4	General Characteristics of Negative-Feedback Amplifiers	417
12-5	Input Resistance	420
12-6	Output Resistance	424
12-7	Method of Analysis of a Feedback Amplifier	426
12-8	Voltage-Series Feedback	428
12-9	A Voltage-Series Feedback Pair	432
12-10	Current-Series Feedback	434
12-11	Current-Shunt Feedback	438
12-12	Voltage-Shunt Feedback	442
	References	444
	Review Questions	445
13	Frequency Response of Amplifiers	447
13-1	Frequency Distortion	447
13-2	Step Response of an Amplifier	451
13-3	Effect of Coupling and Emitter Bypass Capacitors on Low-Frequency Response	445
13-4	The RC-Coupled Amplifier	457
13-5	The Hybrid- π Transistor Model at High Frequencies	458
13-6	Variations of Hybrid- π Parameters	461
13-7	The CE Short-Circuit Current Gain	462
13-8	The Generalized Voltage-Gain Function	464
13-9	Single-Stage CE Transistor Amplifier Response	466
13-10	The Gain-Bandwidth Product	471
13-11	Emitter Follower at High Frequencies	472
13-12	High-Frequency Response of Two Cascaded CE Transistor Stages	475
13-13	Multistage CE Amplifier at High Frequencies	478
13-14	The Common-Source Amplifier at High Frequencies	479

13-15	The Common-Drain Amplifier at High Frequencies	483
13-16	Bandpass of Cascaded Stages	484
	References	486
	Review Questions	486
14	Feedback Amplifier Frequency Response	489
14-1	Effect of Feedback on Amplifier Bandwidth	489
14-2	Double-Pole Transfer Function with Feedback	493
14-3	Three-Pole Transfer Function with Feedback	499
14-4	Approximate Analysis of a Multipole Feedback Amplifier	500
14-5	Voltage-Shunt Feedback Amplifier—Frequency Response	501
14-6	Current-Series Feedback Amplifier—Frequency Response	505
14-7	Current-Shunt Feedback Pair—Frequency Response	508
14-8	Voltage-Series Feedback Pair—Frequency Response	511
14-9	Stability	514
14-10	Bode Plots	516
	References	521
	Review Questions	521
15	Operational Amplifier Characteristics	523
15-1	The Basic Operational Amplifier	523
15-2	The Differential Amplifier	527
15-3	The Emitter-Coupled Differential Amplifier	529
15-4	Transfer Characteristics of a Differential Amplifier	533
15-5	Operational Amplifier Design Techniques	535
15-6	Analog Design Techniques (Continued)	540
15-7	Offset Error Voltages and Currents	546
15-8	Measurement of Operational Amplifier Parameters	551
15-9	Frequency Response of Operational Amplifiers	555
15-10	Compensation	558
15-11	Dominant-Pole Compensation	558
15-12	Pole-Zero Compensation	559
15-13	Lead Compensation	564
	References	565
	Review Questions	566
16	Operational Amplifier Systems	569
16-1	Basic Operational Amplifier Applications	569
16-2	Differential (Instrumentation) Amplifiers	573
16-3	AC-Coupled Amplifier	576
16-4	Analog Integration and Differentiation	577
16-5	Electronic Analog Computation	581
16-6	Active Filters	582
16-7	Active Resonant Bandpass Filters	588
16-8	Precision AC/DC Converters	592
16-9	Sample-and-Hold Systems	596
16-10	Analog Multiplexer and Demultiplexer	599
16-11	Logarithmic and Exponential Amplifier	600

16-12	Digital-to-Analog (D/A) Converters	606
16-13	Analog-to-Digital (A/D) Converters	609
	References	615
	Review Questions	616
17	Waveshaping and Waveform Generators	618
17-1	Comparators	618
17-2	Applications of Comparators	620
17-3	Regenerative Comparator (Schmitt Trigger)	622
17-4	Square-Wave and Triangular-Wave Generators	625
17-5	Pulse Generators	632
17-6	Voltage Time-Base Generators	635
17-7	Step (Staircase) Generators	639
17-8	Modulation of a Square Wave	642
17-9	Sinusoidal Generators	646
17-10	The Phase-Shift Oscillator	649
17-11	A General Form of Oscillator Configuration	651
17-12	The Wien Bridge Oscillator	653
17-13	Crystal Oscillators	655
	References	657
	Review Questions	658
18	Power Circuits and Systems	660
18-1	Large-Signal Amplifiers	660
18-2	Harmonic Distortion	662
18-3	Amplifier Classification	665
18-4	Efficiency of a Class A Amplifier	666
18-5	Class B Push-Pull Amplifiers	667
18-6	Class AB Operation	670
18-7	Integrated-Circuit Power Amplifiers	672
18-8	Thermal Considerations	673
18-9	Regulated Power Supplies	676
18-10	Monolithic Regulators	678
18-11	A Switching Regulator	681
18-12	Additional Switching Regulator Topologies	684
18-13	Power Field-Effect Transistor (VMOS)	689
	References	691
	Review Questions	692
	Appendixes	694
A	Constants and Conversion Factors	694
B	Semiconductor Manufacturers and Device Specifications	696
C	Summary of Network Theory	706
D	Problems	732
E	Answers to Selected Problems	862
	Index	871