

JACOB MILLMAN

**MICRO-
ELECTRONICS**

Digital and Analog Circuits and Systems

MICROELECTRONICS

Digital and Analog
Circuits and Systems

Jacob Millman, Ph.D.
Charles Batchelor Professor, Emeritus
Columbia University

Preface

Prologue: A Brief History of Electronics

Part I Semiconductor Device Characteristics

1 Semiconductors

1-1 Charged Particles

1-2 Field Intensity, Potential, Energy

1-3 Theory of Intrinsic Semiconductors

1-4 Mobility and Conductivity

1-5 Extrinsic and Intrinsic Semiconductors

1-6 Doping and Carrier Concentration

1-7 Recombination and Carrier Lifetime

1-8 Diffusion and Diffusion Coefficient

1-9 Continuity Equation

1-10 Steady-State Diffusion

1-11 Diffusion Current

1-12 Diffusion Length

1-13 Diffusion in a Semiconductor

1-14 Diffusion in a Semiconductor

1-15 Diffusion in a Semiconductor

1-16 Diffusion in a Semiconductor

1-17 Diffusion in a Semiconductor

1-18 Diffusion in a Semiconductor

1-19 Diffusion in a Semiconductor

1-20 Diffusion in a Semiconductor

1-21 Diffusion in a Semiconductor

1-22 Diffusion in a Semiconductor

1-23 Diffusion in a Semiconductor

1-24 Diffusion in a Semiconductor

1-25 Diffusion in a Semiconductor


1-26 Diffusion in a Semiconductor

1-27 Diffusion in a Semiconductor

1-28 Diffusion in a Semiconductor

1-29 Diffusion in a Semiconductor

1-30 Diffusion in a Semiconductor

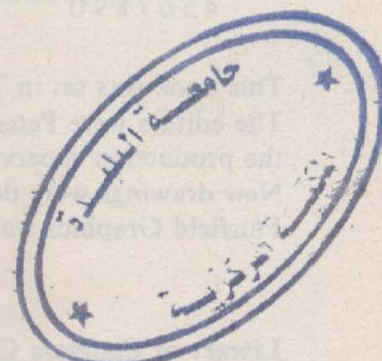

McGraw-Hill Book Company

New York St. Louis San Francisco Auckland Bogotá Düsseldorf
Johannesburg London Madrid Mexico Montreal New Delhi
Panama Paris São Paulo Singapore Sydney Tokyo Toronto

CONTENTS

	Preface	xii
	Prologue: A Brief History of Electronics	xvii
Part 1	Semiconductor Device Characteristics	
1	Semiconductors	1
1-1	Charged Particles	1
1-2	Field Intensity, Potential, Energy	2
1-3	The eV Unit of Energy	4
1-4	Mobility and Conductivity	5
1-5	Electrons and Holes in an Intrinsic Semiconductor	9
1-6	Donor and Acceptor Impurities	12
1-7	Charge Densities in a Semiconductor	14
1-8	Electrical Properties of Ge and Si	15
1-9	The Hall Effect	17
1-10	Thermistors and Sensors	19
1-11	Diffusion	19
1-12	The Potential Variation within a Graded Semiconductor	21
1-13	Recapitulation	23
	References	24
	Review Questions	24
2	Junction-Diode Characteristics	26
2-1	The Open-Circuited p - n Junction	26
2-2	The p - n Junction as a Rectifier	29
2-3	The Volt-Ampere Characteristic	32
2-4	The Temperature Dependence of the V/I Characteristic	35
2-5	Diode Resistance	36
2-6	Space-Charge, or Transition, Capacitance C_T	37
2-7	Minority-Carrier Storage in a Diode	41
2-8	Diffusion Capacitance	44
2-9	Breakdown Diodes	45
2-10	The Diode as a Circuit Element	48
2-11	The Load-Line Concept	49
2-12	The Piecewise Linear Diode Model	50

2-13	Junction-Diode Switching Times	52
	References	54
	Review Questions	55
3	Bipolar Transistor Characteristics	57
3-1	The Junction Transistor	57
3-2	Transistor Current Components	60
3-3	The Transistor as an Amplifier	62
3-4	Transistor Construction	63
3-5	The Common-Base (CB) Configuration	65
3-6	The Common-Emitter (CE) Configuration	68
3-7	The CE Cutoff Currents	73
3-8	The CE Saturation Region	74
3-9	Typical Transistor—Junction Voltage Values	77
3-10	Common-Emitter Current Gain	80
3-11	Inverted Mode of Operation	81
3-12	Transistor Ratings	82
3-13	Additional Transistor Characteristics	85
3-14	Transistor Switching Times	85
	References	88
	Review Questions	88
4	Integrated Circuits: Fabrication and Characteristics	91
4-1	Integrated-Circuit (Microelectronic) Technology	91
4-2	Basic Monolithic Integrated Circuits	93
4-3	Epitaxial Growth	98
4-4	Masking and Etching	98
4-5	Diffusion of Impurities	100
4-6	Transistors for Monolithic Circuits	101
4-7	Monolithic Diodes	105
4-8	The Metal-Semiconductor Contact	107
4-9	Integrated Resistors	109
4-10	Integrated Capacitors	113
4-11	Characteristics of Integrated Components	114
4-12	Monolithic-Circuit Layout	115
4-13	Additional Isolation Methods	118
	References	119
	Review Questions	119
Part 2	Digital Circuits and Systems	
5	Digital Circuits	123
5-1	Digital (Binary) Operation of a System	123
5-2	The OR Gate	125
5-3	The AND Gate	128

5-4	The NOT (INVERTER) Circuit	130
5-5	The INHIBIT (ENABLE) Operation	132
5-6	The EXCLUSIVE-OR Circuit	133
5-7	De Morgan's Laws	135
5-8	The NAND and NOR Diode-Transistor Logic (DTL) Gates	137
5-9	Modified (Integrated-Circuit) DTL Gates	140
5-10	High-Threshold-Logic (HTL) Gate	145
5-11	Transistor-Transistor-Logic (TTL) Gate	146
5-12	Output Stages	148
5-13	Resistor-Transistor Logic (RTL) and Direct-Coupled Transistor Logic (DCTL)	152
5-14	Emitter-Coupled Logic (ECL)	155
5-15	Comparison of Logic Families	160
	References	163
	Review Questions	164
6	Combinational Digital Systems	166
6-1	Standard Gate Assemblies	166
6-2	Binary Adders	169
6-3	Arithmetic Functions	175
6-4	Digital Comparator	177
6-5	Parity Checker/Generator	180
6-6	Decoder/Demultiplexer	181
6-7	Data Selector/Multiplexer	186
6-8	Encoder	189
6-9	Read-Only Memory (ROM)	193
6-10	Two-dimensional Addressing of a ROM	197
6-11	ROM Applications	199
	References	202
	Review Questions	203
7	Sequential Digital Systems	205
7-1	A 1-Bit Memory	205
7-2	The Clocked <i>S-R</i> FLIP-FLOP	208
7-3	<i>J-K</i> , <i>T</i> , and <i>D</i> -Type FLIP-FLOPS	210
7-4	Shift Registers	215
7-5	Ripple (Asynchronous) Counters	220
7-6	Synchronous Counters	225
7-7	Applications of Counters	228
	References	231
	Review Questions	231
8	Field-Effect Transistors	234
8-1	The Junction Field-Effect Transistor	235
8-2	The JFET Volt-Ampere Characteristics	237
8-3	Fabrication of JFETs	241
8-4	The Enhancement Metal-Oxide-Semiconductor Field-Effect Transistor (MOSFET)	242

8-5	The Depletion MOSFET	247
8-6	Technological Improvements	249
8-7	MOSFET Inverters	253
8-8	MOSFET Logic Gates	259
8-9	Complementary MOSFETs	263
	References	267
	Review Questions	267
9	Large-Scale Integration Systems	269
9-1	Dynamic MOS Shift Registers	269
9-2	Ratioless Shift-Register Stages	273
9-3	MOS Read-Only Memory	276
9-4	Erasable-Programmable Read-Only Memory (EPROM)	279
9-5	Programmable Logic Array (PLA)	283
9-6	Random-Access Memory (RAM)	286
9-7	Read/Write Memory Cells	291
9-8	Charge-Coupled Device (CCD)	298
9-9	CCD Structures	302
9-10	CCD Memory Organizations	308
9-11	Microprocessor and Microcomputer	312
9-12	Integrated-Injection Logic (I^2L)	315
9-13	Injection Logic Circuits	321
	References	325
	Review Questions	326

Part 3 Analog Circuits and Systems

10	Analog Diode Circuits	333
10-1	A Simple Application	333
10-2	Clipping (Limiting) Circuits	335
10-3	Clipping at Two Independent Levels	338
10-4	A Breakdown-Diode Voltage Regulator	342
10-5	Rectifiers	343
10-6	Other Full-Wave Circuits	348
10-7	Capacitor Filters	350
10-8	Additional Diode Circuits	354
	Reference	356
	Review Questions	356
11	Low-Frequency Amplifiers	358
11-1	The Operating Point of a BJT	359
11-2	Bias Stability	361
11-3	Self-Bias or Emitter Bias	363
11-4	Stabilization against Variations in I_{CO} , V_{BE} , and β	365
11-5	Output Waveforms for a Sinusoidal Input	370
11-6	Approximate Small-Signal BJT Models	372
11-7	The Transistor Transconductance	373

11-8	Linear Analysis of a Transistor Circuit	375
11-9	The Common-Emitter (CE) Amplifier	376
11-10	The Emitter Follower	379
11-11	The Common-Base (CB) Amplifier	381
11-12	Comparison of BJT Amplifier Configurations	381
11-13	The CE Amplifier with an Emitter Resistor	382
11-14	Cascading Transistor Amplifiers	384
11-15	Accurate Small-Signal BJT Models	389
11-16	High-Input-Resistance BJT Circuits	393
11-17	Biasing the Field-Effect Transistor	397
11-18	The JFET or MOSFET Small-Signal Model	400
11-19	The Low-Frequency Common-Source and Common-Drain Amplifiers	402
11-20	The JFET as a Voltage-Controlled Resistor (VCR)	405
	References	406
	Review Questions	406
12	Feedback Amplifier Characteristics	409
12-1	Classification of Amplifiers	409
12-2	The Feedback Concept	411
12-3	The Transfer Gain with Feedback	414
12-4	General Characteristics of Negative-Feedback Amplifiers	417
12-5	Input Resistance	420
12-6	Output Resistance	424
12-7	Method of Analysis of a Feedback Amplifier	426
12-8	Voltage-Series Feedback	428
12-9	A Voltage-Series Feedback Pair	432
12-10	Current-Series Feedback	434
12-11	Current-Shunt Feedback	438
12-12	Voltage-Shunt Feedback	442
	References	444
	Review Questions	445
13	Frequency Response of Amplifiers	447
13-1	Frequency Distortion	447
13-2	Step Response of an Amplifier	451
13-3	Effect of Coupling and Emitter Bypass Capacitors on Low-Frequency Response	445
13-4	The RC -Coupled Amplifier	457
13-5	The Hybrid- π Transistor Model at High Frequencies	458
13-6	Variations of Hybrid- π Parameters	461
13-7	The CE Short-Circuit Current Gain	462
13-8	The Generalized Voltage-Gain Function	464
13-9	Single-Stage CE Transistor Amplifier Response	466
13-10	The Gain-Bandwidth Product	471
13-11	Emitter Follower at High Frequencies	472
13-12	High-Frequency Response of Two Cascaded CE Transistor Stages	475
13-13	Multistage CE Amplifier at High Frequencies	478
13-14	The Common-Source Amplifier at High Frequencies	479

13-15	The Common-Drain Amplifier at High Frequencies	483
13-16	Bandpass of Cascaded Stages	484
	References	486
	Review Questions	486
14	Feedback Amplifier Frequency Response	489
14-1	Effect of Feedback on Amplifier Bandwidth	489
14-2	Double-Pole Transfer Function with Feedback	493
14-3	Three-Pole Transfer Function with Feedback	499
14-4	Approximate Analysis of a Multipole Feedback Amplifier	500
14-5	Voltage-Shunt Feedback Amplifier—Frequency Response	501
14-6	Current-Series Feedback Amplifier—Frequency Response	505
14-7	Current-Shunt Feedback Pair—Frequency Response	508
14-8	Voltage-Series Feedback Pair—Frequency Response	511
14-9	Stability	514
14-10	Bode Plots	516
	References	521
	Review Questions	521
15	Operational Amplifier Characteristics	523
15-1	The Basic Operational Amplifier	523
15-2	The Differential Amplifier	527
15-3	The Emitter-Coupled Differential Amplifier	529
15-4	Transfer Characteristics of a Differential Amplifier	533
15-5	Operational Amplifier Design Techniques	535
15-6	Analog Design Techniques (Continued)	540
15-7	Offset Error Voltages and Currents	546
15-8	Measurement of Operational Amplifier Parameters	551
15-9	Frequency Response of Operational Amplifiers	555
15-10	Compensation	558
15-11	Dominant-Pole Compensation	558
15-12	Pole-Zero Compensation	559
15-13	Lead Compensation	564
	References	565
	Review Questions	566
16	Operational Amplifier Systems	569
16-1	Basic Operational Amplifier Applications	569
16-2	Differential (Instrumentation) Amplifiers	573
16-3	AC-Coupled Amplifier	576
16-4	Analog Integration and Differentiation	577
16-5	Electronic Analog Computation	581
16-6	Active Filters	582
16-7	Active Resonant Bandpass Filters	588
16-8	Precision AC/DC Converters	592
16-9	Sample-and-Hold Systems	596
16-10	Analog Multiplexer and Demultiplexer	599
16-11	Logarithmic and Exponential Amplifier	600

16-12	Digital-to-Analog (D/A) Converters	606
16-13	Analog-to-Digital (A/D) Converters	609
	References	615
	Review Questions	616
17	Waveshaping and Waveform Generators	618
17-1	Comparators	618
17-2	Applications of Comparators	620
17-3	Regenerative Comparator (Schmitt Trigger)	622
17-4	Square-Wave and Triangular-Wave Generators	625
17-5	Pulse Generators	632
17-6	Voltage Time-Base Generators	635
17-7	Step (Staircase) Generators	639
17-8	Modulation of a Square Wave	642
17-9	Sinusoidal Generators	646
17-10	The Phase-Shift Oscillator	649
17-11	A General Form of Oscillator Configuration	651
17-12	The Wien Bridge Oscillator	653
17-13	Crystal Oscillators	655
	References	657
	Review Questions	658
18	Power Circuits and Systems	660
18-1	Large-Signal Amplifiers	660
18-2	Harmonic Distortion	662
18-3	Amplifier Classification	665
18-4	Efficiency of a Class A Amplifier	666
18-5	Class B Push-Pull Amplifiers	667
18-6	Class AB Operation	670
18-7	Integrated-Circuit Power Amplifiers	672
18-8	Thermal Considerations	673
18-9	Regulated Power Supplies	676
18-10	Monolithic Regulators	678
18-11	A Switching Regulator	681
18-12	Additional Switching Regulator Topologies	684
18-13	Power Field-Effect Transistor (VMOS)	689
	References	691
	Review Questions	692
	Appendixes	694
A	Constants and Conversion Factors	694
B	Semiconductor Manufacturers and Device Specifications	696
C	Summary of Network Theory	706
D	Problems	732
E	Answers to Selected Problems	862
	Index	871