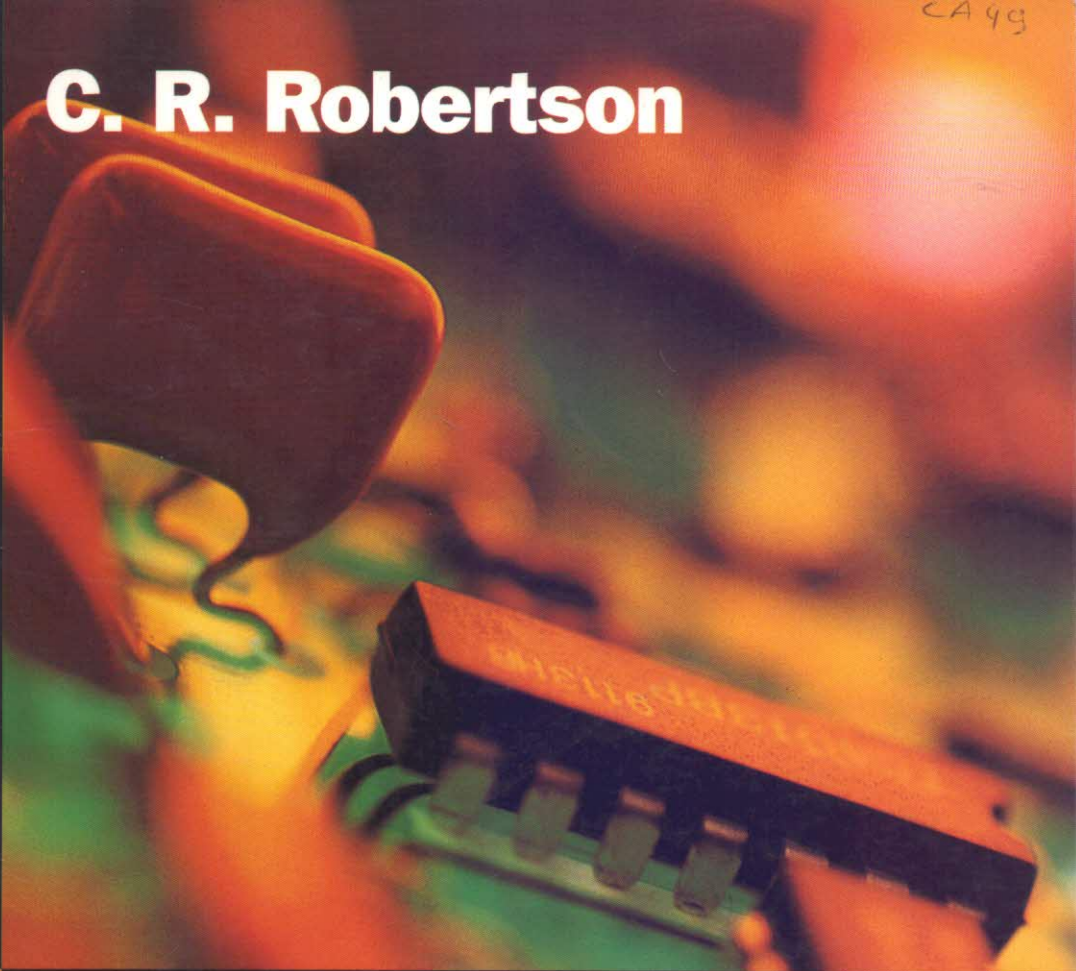


CA 99
C. R. Robertson



**Fundamental
Electrical
& Electronic
Principles**

Contents

<i>Preface</i>	xi
<i>Introduction</i>	xii
1 Fundamentals	1
Units	1
Standard Form Notation	2
'Scientific' Notation	2
Conversion of Areas and Volumes	4
Graphs	5
Basic Electrical Concepts	7
Communication	23
Assignment Questions	26
Supplementary Worked Examples	27
Summary of Equations	33
2 D.C. Circuits	34
Resistors in Series	34
Resistors in Parallel	39
Potential Divider	44
Current Divider	45
Series/Parallel Combinations	47
Kirchhoff's Current Law	50
Kirchhoff's Voltage Law	52
Other Network Theorems	56
Superposition Theorem	56
Constant Voltage and Constant Current Sources and their Equivalence	58
Thévenin's Theorem	61
Norton's Theorem	65
The Maximum Power Transfer Theorem	68
The Decibel and its Usage	70
The Wheatstone Bridge Network	76
The Wheatstone Bridge Instrument	83
The Slidewire Potentiometer	85
Assignment Questions	87

Suggested Practical Assignments	96
Supplementary Worked Examples	99
Summary of Equations	122
3 Electric Fields and Capacitors	123
Coulomb's Law	123
Electric Fields	124
Electric Field Strength	126
Electric Flux and Flux Density	126
The Charging Process and Potential Gradient	127
Capacitance	130
Capacitors	130
Permittivity of Free Space	131
Relative Permittivity	131
Absolute Permittivity	131
Calculating Capacitor Values	132
Capacitors in Parallel	134
Capacitors in Series	136
Series/Parallel Combinations	140
Multiplate Capacitors	142
Energy Stored	144
Dielectric Strength and Working Voltage	147
Capacitor Types	148
Assignment Questions	151
Suggested Practical Assignment	155
Supplementary Worked Examples	155
Summary of Equations	162
4 Magnetic Fields and Circuits	163
Magnetic Materials	163
Magnetic Fields	163
The Magnetic Circuit	166
Magnetic Flux and Flux Density	167
Magnetomotive Force	168
Magnetic Field Strength	170
Permeability of Free Space	171
Relative Permeability	171
Absolute Permeability	171
Magnetisation (B/H) Curve	173
Composite Series Magnetic Circuits	177
Reluctance	180
Comparison of Electrical, Magnetic and Electrostatic Quantities	184
Magnetic Hysteresis	185
Parallel Magnetic Circuits	187
Assignment Questions	187
Suggested Practical Assignments	189

Supplementary Worked Examples	192
Summary of Equations	196

5 Electromagnetism	197
Faraday's Law of Electromagnetic Induction	197
Lenz's Law	199
Fleming's Righthand Rule	200
EMF Induced in a Single Straight Conductor	203
Force on a Current-Carrying Conductor	207
The Motor Principle	209
Force between Parallel Conductors	211
The Moving Coil Meter	215
Shunts and Multipliers	218
Shunts	218
Multipliers	219
Figure of Merit and Loading Effect	221
The Ohmmeter	223
Wattmeter	224
Eddy Currents	226
Self and Mutual Inductance	227
Self-Inductance	228
Self-Inductance and Flux Linkages	230
Factors Affecting Inductance	232
Mutual Inductance	234
Relationship between Self- and Mutual-Inductance	235
Energy Stored	236
The Transformer Principle	237
Transformer Voltage and Current Ratios	239
Assignment Questions	242
Suggested Practical Assignments	246
Supplementary Worked Examples	249
Summary of Equations	257
6 Alternating Quantities	259
Production of an Alternating Waveform	259
Angular Velocity and Frequency	262
Standard Expression for an Alternative Quantity	262
Average Value	265
r.m.s. Value	266
Peak Factor	266
Form Factor	267
Rectifiers	269
Half-wave Rectifier	270
Full-wave Bridge Rectifier	271
Rectifier Moving Coil Meter	273
Phase and Phase Angle	275

Phasor Representation	277
Addition of Alternating Quantities	279
The Cathode Ray Oscilloscope	284
Operation of the Oscilloscope	286
Dual Beam Oscilloscopes	288
Assignment Questions	289
Suggested Practical Assignments	292
Supplementary Worked Examples	292
Summary of Equations	296
7 Single Phase a.c. Circuits	297
Pure Resistance	297
Pure Inductance	299
Inductive Reactance	301
Pure Capacitance	304
Capacitive Reactance	306
Impedance	310
Inductance and Resistance in Series	310
Resistance and Capacitance in Series	316
Resistance, Inductance and Capacitance in Series	319
Power in the a.c. Circuit	323
Power Factor	323
Power Triangle	324
Series Resonance	326
Assignment Questions	330
Suggested Practical Assignments	333
Supplementary Worked Examples	336
Summary of Equations	344
8 Control Principles	345
Introduction	345
Non-engineering Applications	345
Engineering Applications	346
Classification of Control Systems	346
Open-loop Systems	347
Closed-loop Systems	348
Transfer Functions and Block Diagrams	351
A Positional Control System	354
System Response and Stability	355
Assignment Questions	357
9 Semiconductor Theory and Devices	358
Atomic Structure	358
Intrinsic (pure) Semiconductors	359
Electron-Hole Pair Generation and Recombination	361

Conduction in Intrinsic Semiconductors	362
Extrinsic (Impure) Semiconductors	363
n-type Semiconductor	363
p-type Semiconductor	364
The p-n Junction	366
The p-n Junction Diode	367
Forward-biased Diode	367
Reverse-biased Diode	368
Diode Characteristics	369
The Bipolar Junction Transistor (BJT)	370
Transistor Circuit Configurations	372
BJT Common Emitter Characteristics	373
BJT Common Base Characteristics	377
Relationship Between h_{FE} and h_{FB}	381
The Unipolar Junction Transistor (UJT)	382
The JUGFET	382
n-channel JUGFET Characteristics	383
JUGFET Parameters	384
The Metal-Oxide Semiconductor Transistor (MOSFET)	387
Depletion Mode MOSFET	388
Comparison of FETs with BJTs	391
Assignment Questions	391
Suggested Practical Assignments	392
Summary of Equations	393
10 Semiconductor Circuits	394
The Zener Diode	394
Transistor Bias	398
A Simple Bias Circuit	399
Thermal Runaway	401
Bias with Thermal Stabilisation	402
Three-resistor Bias and Stabilisation	402
Biasing Circuits for FETs	404
Small-signal a.c. Amplifiers	405
Three-resistor-biased Amplifier Circuit	414
FET Small-signal Amplifier	417
The Transistor as a Switch	421
Assignment Questions	423
Suggested Practical Assignments	427
Supplementary Worked Examples	430
Summary of Equations	434
<i>Answers to Assignment Questions</i>	435
<i>Appendix A: SI Units and Quantities</i>	441
<i>Index</i>	443