



OPERATIONAL AMPLIFIERS

Second Edition

Arpad Barna

Dan I. Porat

Contents

CHAPTER 1

Operational Amplifiers

1.1 Properties

1.2 Applications

Problems

CHAPTER 2

Ideal Operational Amplifiers

2.1 Noninverting Amplifiers

2.2 Inverting Amplifiers

2.3 Differential Amplifiers

2.4 Floating-Input Differential Amplifiers

Problems

CHAPTER 3

Feedback

3.1 Noninverting Feedback Amplifiers

3.2 Inverting Feedback Amplifiers

3.3 Differential Feedback Amplifiers

3.4 Voltage Followers

3.5 Instrumentation Amplifiers

Problems

CHAPTER 4

Accuracy of the Amplification

4.1 Small Variations in Operational Amplifier Amplification

4.2 Small Variations in the Feedback Resistor

4.3 Small Variations in the Input Resistor

4.4 Several Sources of Variations

Problems

1

2

3

3

5

5

6

6

7

8

11

11

13

15

19

19

21

27

28

30

33

33

35

CHAPTER 5

Frequency Response and Transient Response of Operational Amplifiers, Part I 39

5.1 Lag Networks 39

5.2 Bode Plots 44

5.3 Cascaded Lag Networks 45

Problems 55

CHAPTER 6

Frequency Response and Transient Response of Operational Amplifiers, Part II 59

6.1 Modified Lag Networks 59

6.2 Lead Networks 63

6.3 Voltage Divider Networks 66

6.4 Compound Lag Networks 70

6.5 Series RLC Circuits 76

Problems 80

CHAPTER 7

Stability of Feedback Amplifiers 83

7.1 The Nyquist Criterion 83

7.2 Lag Networks 87

7.3 Lag Compensation 94

7.4 Lead-Lag Compensation 96

7.5 Conditional Stability 98

7.6 Phase Margins 99

7.7 Inverting Feedback Amplifiers 114

Problems 115

CHAPTER 8

Frequency Response and Transient Response of Feedback Amplifiers 119

8.1 Operational Amplifiers with $A = A_{dc} = \infty$ 119

8.2 Operational Amplifiers with $A = A_{dc}/(1 + jf/f_1)$ 123

8.3 Operational Amplifiers with $A = A_{dc}/[(1 + jf/f_1)(1 + jf/f_2)]$ 135

8.4 Operational Amplifiers with $A = A_{dc}/[(1 + jf/f_1)(1 + jf/f_2)(1 + jf/f_3)]$ 166

8.5 Inverting Feedback Amplifiers 182

8.6 Computer-Aided Design 184

Problems 185

CHAPTER 9**Properties of Real Operational Amplifiers, Part I**

| | |
|---|-----|
| 9.1 Common-Mode Amplification and Common-Mode Rejection | 197 |
| 9.2 Input Impedances | 202 |
| 9.3 Output Impedance | 205 |
| 9.4 Supply-Voltage Rejection | 207 |
| Problems | 208 |

CHAPTER 10**Properties of Real Operational Amplifiers, Part II**

| | |
|------------------------------|-----|
| 10.1 Input Currents | 209 |
| 10.2 Input Offset Voltage | 211 |
| 10.3 Limitations and Ratings | 212 |
| 10.4 Slew Rate | 214 |
| 10.5 Noise | 215 |
| Problems | 217 |

CHAPTER 11**Other Circuits**

| | |
|------------------------------|-----|
| 11.1 Current Source Inputs | 219 |
| 11.2 Adder Circuits | 223 |
| 11.3 Integrator Circuits | 225 |
| 11.4 Differentiator Circuits | 237 |
| 11.5 Nonlinear Circuits | 239 |
| Problems | 240 |

CHAPTER 12**Internal Structure**

| | |
|----------------------|-----|
| 12.1 Input Stages | 245 |
| 12.2 Current Mirrors | 247 |
| 12.3 Output Stages | 252 |
| Problems | 253 |

APPENDIX A**Mathematical Equations**

| | |
|-----------------------------|-----|
| A.1 Quadratic Equations | 255 |
| A.2 Cubic Equations | 255 |
| A.3 Laplace Transform Pairs | 257 |

APPENDIX B

Derivations

- B.1 Proof of Equations 6.31a-e
- B.2 The Relative Magnitudes of τ_L , τ_2 , and τ_U

259

259

264

APPENDIX C

Properties of Operational Amplifiers Used in the Examples and Problems

267

Answers to Selected Problems

269

Index

271