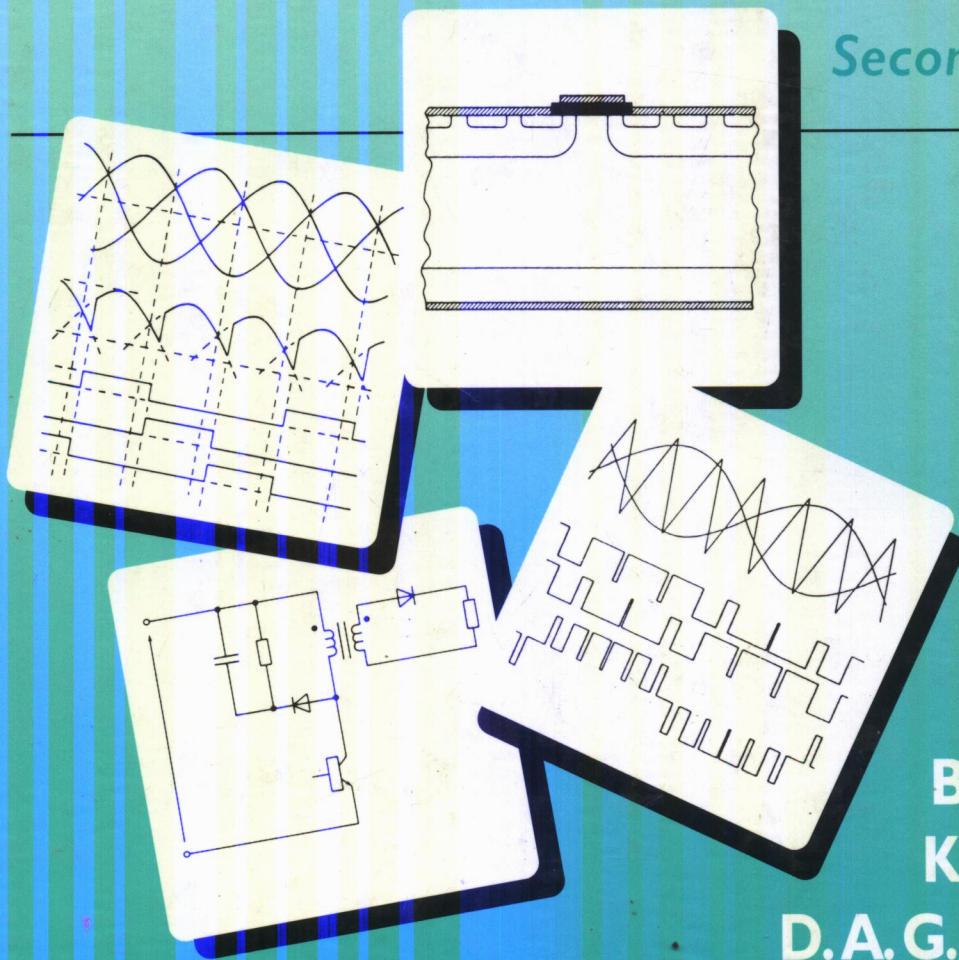


An Introduction to **P·O·W·E·R·** **ELECTRONICS**

Second Edition



B. M. BIRD
K. G. KING
D. A. G. PEDDER



WILEY

Publishers Since 1807

CONTENTS

Preface to the First Edition	xi
Preface to the Second Edition	xiii
Symbols	xv
Subscripts	xvii
Chapter 1 Power Semiconductor Devices	1
The p–n Junction	2
The Transistor	5
The power MOSFET	7
The insulated-gate bipolar transistor (IGBT)	9
The cascade switch	11
The Thyristor	13
Mechanical construction	15
The Switching Behaviour of Diodes and Thyristors	16
The turn-on process in thyristors	18
Turn-off processes	20
Reverse recovery	21
Forced Commutation	22
Forced commutation with substantial reverse voltage	23
Determination of commutating capacitance	24
Commutation with inverse-parallel diode	26
Characteristics and Ratings of Diodes and Thyristors	29
Effects of temperature	30
Voltage ratings	31
Forward current rating	33
Gate firing characteristics and gate ratings	35
Holding and latching currents	37
di/dt	38
dv/dt	39
Special Thyristor Structures	41
Shorted emitter	41
Amplifying gate	42
Asymmetrical thyristor	43
The gate turn-off thyristor (GTO)	43
Bi-directional thyristors	45

Chapter 2 Naturally Commutating Converters	47
Definitions	47
The Single-phase Half-wave Rectifier	48
Multi-phase Single-way Rectifiers	51
Commutation in multi-phase rectifiers	53
D.C. output voltage and a.c. input current	53
Practical forms of single-way rectifier	54
The utilization of compounds in simple single-way rectifiers	59
Input current harmonics	62
The relationship of transformer utilization and current waveforms	63
Input power factor	64
Multiplex Single-way Rectifiers	65
The hexaphase rectifier with interphase reactor	68
Magnetizing current in the interphase reactor	70
Phase Multiplication and Input Harmonics	71
12-pulse and 24-pulse Rectifiers	73
Bridge Rectifiers	74
Three-phase Bridge Rectifier	75
Single-phase Bridge Rectifier	78
Multiplex Bridge Rectifiers	79
General Comparison of Rectifier Circuits	81
Controlled Converters	81
Input harmonics, power factor and transformer utilization	84
Multiplex and Bridge Converters	85
The Half-controlled Bridge	86
Input current	88
Input power factor of half-controlled bridges	89
Controlled Rectifiers with Free-wheel Diodes	92
Single-way rectifier	93
Bridge rectifier with free-wheel diode	95
Input characteristics of controlled rectifiers with free-wheel diodes	96
Two-bridge Half-controlled Rectifier	97
Generalized Output Waveforms and Ripple Voltage	98
Output ripple from half-controlled bridge rectifiers	102
Controlled rectifiers with free-wheel diodes	105
Interphase Reactor Rating in Controlled Converters	106
Operation of Converters with Finite Source Inductance	107
Single-way converters	107
Voltage-time integrals and voltage drop	108
Overlap angle	109
Overlap in bridge converters	111
Half-controlled bridge rectifiers with finite source inductance	113
Relationships between per-unit reactance and voltage drop	113
Overlap during inversion: loss of communication	114
Loss of commutation in half-controlled rectifiers	117
Reduction of input harmonics due to overlap	118
Effect of overlap on output ripple	121
Smoothing	122
Critical inductance	123
Uncontrolled rectifier	125
Controlled converter with smooth output voltage	127
Controlled converter with LR load	129
Discontinuous-current Characteristics	130
Controlled converters	131
Uncontrolled rectifiers	134
Overload and Short-circuit Characteristics of Rectifiers	134

	Single-phase rectifiers	135
	Three-phase single-way rectifier	136
	Three-phase bridge rectifier	137
	Multiplex rectifiers	137
	Total Voltage Drop	138
	Weighted ripple	139
	Applications of Converters: Double Converters	140
	Appendix 2(i) Two-pulse Rectifier with Capacitive Load	142
	Appendix 2(ii) The Overall Power Factor of Rectifier Equipment	143
	Appendix 2(iii) Analysis of Input Current Waveform of a Three-phase Bridge Rectifier	145
	Problems	149
Chapter 3	A.C. Regulators	151
	Single-phase Regulator	151
	Three-phase A.C. Regulators	153
	Three-phase three-wire a.c. regulators	154
	Thyristor–diode regulators	157
	Open-star regulators	158
	Thyristor voltage ratings	160
	Regulators with Inductive Load	161
	A.C. Regulators Conjoined with Rectifiers	163
	Input Power Factor and Harmonics	164
	Integral-half-cycle Control	166
	Thyristor Tap-changers	169
	Problems	171
Chapter 4	D.C. Switching Regulators	173
	Harmonic content of output and input	177
	Practical step-down regulator	179
	Discontinuous output current	180
	Regulator without voltage smoothing	182
	Modes of control	184
	Step-up Regulators	184
	The Step-up/Step-down or Buck-boost Converter	189
	Continuous-mode operation	189
	Discontinuous-mode operation	190
	Circuit applications	191
	The Ćuk converter	192
	Bi-directional and Four-quadrant Regulators	193
	Multi-phase Switching Regulators	195
	Commutation Circuits	198
	Commutation with inverse parallel diode	206
	Switching regulators without auxiliary thyristors	208
	Two- and four-quadrant regulators	210
	Converters Having Isolation between Input and Output	210
	The forward converter	210
	Flyback or energy storage converter	214
	Other isolated converters	220
	Off-line Switched-mode Power Supplies	221
	Appendix 4(i) Fourier Analysis of Switching Regulator Waveforms	223
	Problems	224

Chapter 5 Static Power Inverters

Voltage-fed Inverters	229
Basic operation	230
Reactive feedback diodes	230
Bridge inverter with inductive load	231
Bridge inverter with leading load	232
Three-phase bridge inverter	236
Methods of forced commutation	237
The McMurray inverter	241
The bi-phase inverter	241
Output voltage control	243
Voltage control in three-phase inverters	244
Output voltage harmonics	247
Reduction of output harmonics	249
Phase multiplication	251
Multiple pulse-width control	254
Selected harmonic reduction	255
Pulse-width modulation	259
Current-fed Inverters	261
Operation with significant turn-off time	264
Operation in practice	266
Untuned parallel inverters	267
Variation of output voltage with load	268
Reactive feedback in current-fed inverters	270
Control of circulating current	271
Further current-fed inverter configurations	272
Comparison of Inverter Techniques	275
Appendix 5(i) Characteristics of Resonant Loads	278
Appendix 5(ii) McMurray Commutation Circuit	279
Appendix 5(iii) Fourier Analysis of Rectilinear Waveforms	281
Appendix 5(iv) Output Voltage of Simple Current-fed Inverter with CR Load	286
Appendix 5(v) Commutation in Current-fed Inverters with Reactive Feedback	287
Appendix 5(vi) Harmonics Generated by Sinusoidal P.W.M. in a Bridge Inverter	288
Problems	291
	293

Chapter 6 Application Techniques

Cooling of Semiconductor Devices	295
Mounting of semiconductor devices	295
Air coolers	296
Natural air cooling	297
Forced air cooling	297
Thermal time response	298
Multiple cooler assemblies	298
Liquid cooling	299
The Estimation of Instantaneous Temperature in Semiconductor Devices	300
Single rectangular pulse	300
Repeated rectangular pulse	302
Extended train of similar rectangular pulses	303
Single pulse of other than rectangular waveform	304
Extended train of pulses of other than rectangular waveform	306
Overcurrent Protection in Thyristor and Diode Circuits	307
	308

Overcurrent protection by fuses	310
Matching of thyristors and fuses in a.c. circuits	313
Fuses in d.c. circuits	316
Fuses in series and parallel	316
Automatic current limiting	316
dv/dt Suppression	317
Overvoltage Protection	320
Transformer switching surges	320
Protection of switching converters and regulators against internally generated transients	324
The CRD dissipative snubber	326
The energy-recovery snubber	328
Turn-on snubbers	330
Passive flux resetting circuit for transformer-coupled converters	330
Supply-borne transients	334
Rectifier-fed suppression capacitors	334
Surge voltages due to carrier storage	335
Non-linear surge suppressors	335
Crowbar circuits	337
Series Operation of Diodes and Thyristors	337
Steady-state voltage sharing	338
Transient voltage sharing	339
Reverse recovery	339
Variations in turn-on time	340
Overall design of sharing networks	342
Selection of cells for series operation	342
Parallel Operation of Diodes and Thyristors	343
Current sharing in diodes and thyristors	343
Current sharing with individual inductors	344
Firing parallel-connected thyristors	348
The Firing of Thyristors	349
Gate current amplitude and rise time	349
Gate pulse duration	350
Pulse waveforms	351
Spurious triggering	352
Firing-angle determination in naturally commutating converters	352
Variable phase shift	352
Magnetic amplifiers	353
Waveform-intersection systems	353
Digital systems	354
Additional design features	354
Appendix 6(i) Basic Heat-transfer Relationships	354
Appendix 6(ii) Response of Damped <i>LCR</i> Circuits	356
Problems	360
Bibliography	363
Answers to Problems	365
Index	367