

# EXPERIMENTAL ELECTRONICS FOR STUDENTS

K.J. Close    J. Yarwood



# Contents

	Preface	page v
1	Introductory General Notes	1
1.1	Soldering components to interconnections when utilizing strip board	1
1.2	Resistor colour code	3
1.3	Symbols used in circuit diagrams	4
1.4	Symbols for quantities	5
1.5	Abbreviations	5
1.6	Notes on some aspects of electrical measuring instruments	7
2	Semiconductor Diodes: Characteristics; Use in D.C. Power Supplies	12
2.1	Semiconductor diodes	12
	2.1.1 Characteristics of a p-n junction diode	13
	2.1.2 Determination of $e/k$	14
	2.1.3 Questions	15
	2.1.4 Further investigations	15
2.2	Zener diodes	16
	2.2.1 The reverse characteristic of a Zener diode	17
	2.2.2 Question	18
2.3	D.C. power supplies: an introduction	18
	2.3.1 Half-wave rectifier	18
	2.3.2 Half-wave rectifier with reservoir smoothing capacitor	20
	2.3.3 Full-wave rectifier, transformer and bridge circuits	22
	2.3.4 Full-wave rectifier with smoothing capacitor	22
	2.3.5 Zener diode across a full-wave rectifier circuit	23
	2.3.6 Zener diode stabilization	24
	2.3.7 Question	25

## CONTENTS

	2.3.8 Further investigations	25
3	Bipolar Junction Transistors: Characteristics and Simple Associated Circuits	26
3.1	Bipolar junction transistors	26
3.2	Characteristics of an n-p-n transistor in common-base (CB) connection	26
	3.2.1 Output characteristics and output conductance $h_{ob}$	27
	3.2.2 The current gain	28
	3.2.3 Power considerations	29
	3.2.4 More accurate value of $h_{ob}$	29
3.3	Characteristics of an n-p-n bipolar transistor in common-emitter (CE) connection	30
	3.3.1 Output characteristics and the output conductance $h_{oe}$	30
	3.3.2 The current gain $h_{fe}$	31
	3.3.3 Power dissipation	31
3.4	A bipolar transistor tester	32
3.5	Further investigation	35
3.6	Voltage stabilizing circuits: general information; the use of bipolar transistors	35
	3.6.1 Emitter follower voltage stabilizer	36
3.7	Constant current sources: introduction	38
	3.7.1 A constant current source based on a bipolar junction transistor	38
	3.7.2 Further investigations	40
3.8	Amplifiers: use of bipolar transistors	41
	3.8.1 A common-emitter (CE) bipolar transistor single-stage amplifier	43
3.9	Sinusoidal waveform generators	49
	3.9.1 A phase-shift sinusoidal oscillator based on a bipolar transistor	51
	3.9.2 A crystal-controlled sinusoidal oscillator	52
	3.9.3 A Wien bridge oscillator	53
3.10	Multivibrators	57
	3.10.1 The stable (free-running) multivibrator	57
	3.10.2 Effect of varying the applied voltage on the period of a free-running multivibrator	58
	3.10.3 A gated free-running multivibrator	60
	3.10.4 The monostable multivibrator	60
	3.10.5 A monostable multivibrator utilizing bipolar transistors for experimental work	64
	3.10.6 The bistable multivibrator	65
	3.10.7 A bistable multivibrator based on bipolar transistors	67
3.11	The Schmitt trigger circuit	68

3.12	Sweep generator: utilizing the bootstrap principle	70
3.13	An optically-coupled isolator	72
3.13.1	Output characteristics of the phototransistor	73
3.13.2	Current transfer ratio	75
3.13.3	Photodiode operation	75
3.13.4	Switching characteristic	76
3.13.5	Questions	76
3.14	A typical application of an optically-coupled isolator	77
4	Field Effect Transistors: Characteristics and Simple Associated Circuits	78
4.1	Field-effect transistors (FETs or fets)	78
4.1.1	The drain characteristics	80
4.1.2	The effect of temperature on the drain current $I_D$	80
4.1.3	Use as a voltage-controlled resistance	81
4.1.4	The transfer characteristic	82
4.1.5	Automatic bias; provision of gate-source bias by means of a source resistor	83
4.1.6	Demonstration of the high input resistance of a fet	84
4.1.7	Further investigation	85
4.2	A simple common-source fet amplifier	85
4.2.1	The voltage gain of a fet amplifier	86
4.3	Sinusoidal waveform generators based on field-effect transistors	87
4.4	Multivibrators utilizing fets	87
4.4.1	A free-running multivibrator based on the use of n-channel fets	87
4.4.2	A hybrid free-running multivibrator	88
4.4.3	A voltage-to-frequency converter based on a free-running multivibrator utilizing field-effect transistors	89
4.4.4	A monostable multivibrator with a pulse width determined by a fet-based constant current source	90
5	Unijunction Transistors; Silicon Controlled Rectifiers: Characteristics and Applications	91
5.1	Unijunction transistors (UJT's or ujt's)	91
5.1.1	The intrinsic stand-off ratio	92
5.2	Relaxation oscillators	93
5.2.1	A relaxation oscillator based on a unijunction transistor	93
5.3	A staircase generator or frequency divider based on a unijunction transistor	94
5.4	Programmable unijunction transistors (PUTs or puts)	95

## CONTENTS

5.4.1	<i>Selection of the value of the intrinsic stand-off ratio with a put</i>	96
5.5	<i>A relaxation oscillator based on a put</i>	96
5.6	<i>Silicon controlled rectifiers (SCRs or scrs)</i>	97
5.7	<i>Phase control by means of silicon controlled rectifiers</i>	99
5.7.1	<i>Half-wave phase control with a phase angle between 0 and <math>\pi/2</math></i>	100
5.7.2	<i>Half-wave phase control with a phase angle between 0 and <math>\pi</math></i>	101
5.7.3	<i>Questions</i>	101
5.8	<i>Phase control by means of an scr fired by pulses from a ujt circuit</i>	101
5.8.1	<i>Phase control utilizing two scrs</i>	102
5.8.2	<i>Alternative control of the phase angle</i>	103
5.8.3	<i>Utilizing a ujt firing circuit with simple negative feedback</i>	104
5.8.4	<i>Further investigations</i>	105
5.9	<i>Phase control by means of a put</i>	105
5.10	<i>A bistable circuit based on the use of silicon controlled rectifiers</i>	106
6	<i>More Complex Amplifiers and some Applications</i>	110
6.1	<i>Differential or difference amplifiers</i>	110
6.1.1	<i>To determine the similarity between two fets fabricated on the same silicon substrate</i>	114
6.1.2	<i>The phase relationships in the differential amplifier</i>	115
6.1.3	<i>The paraphase amplifier</i>	116
6.1.4	<i>The differential voltage gain <math>A_d</math></i>	116
6.1.5	<i>The common-mode voltage gain <math>A_c</math></i>	117
6.1.6	<i>The common-mode rejection ratio (cmrr)</i>	118
6.1.7	<i>Use of a constant current source to replace <math>R_S</math></i>	119
6.1.8	<i>Questions</i>	120
6.2	<i>Operational amplifiers</i>	121
6.2.1	<i>The closed-loop gain of the inverting configuration</i>	123
6.2.2	<i>The closed-loop gain of the non-inverting configuration</i>	124
6.2.3	<i>The operational amplifier as a sign inverter</i>	124
6.2.4	<i>The gain control in the inverting configuration</i>	125
6.2.5	<i>Further investigation</i>	126
6.2.6	<i>The frequency response of the amplifier in the inverting configuration</i>	126
6.2.7	<i>The closed-loop gain in the non-inverting configuration</i>	127

6.2.8	<i>Frequency response in the non-inverting configuration</i>	128
6.2.9	<i>Simultaneous product and sum</i>	128
6.2.10	<i>Comment</i>	129
6.2.11	<i>Integrated circuit operational amplifiers</i>	129
6.2.12	<i>Transfer characteristic of the amplifier in the inverting configuration</i>	132
6.2.13	<i>Frequency response of the amplifier in the inverting configuration</i>	134
6.2.14	<i>Slew rate limiting of the amplifier</i>	135
6.2.15	<i>A logarithmic amplifier</i>	137
6.2.16	<i>Measurement of the input bias currents and the offset voltage of an operational amplifier</i>	140
6.3	<i>Applications of operational amplifiers</i>	142
6.3.1	<i>Use of an operational amplifier to current drive a meter</i>	142
6.3.2	<i>The operational integrator and its use as a ramp generator</i>	143
6.3.3	<i>Questions</i>	145
6.3.4	<i>A squaring circuit</i>	145
6.3.5	<i>A free-running multivibrator based on the use of an operational amplifier</i>	146
6.3.6	<i>Sensitivity of the frequency of the free-running multivibrator based on an operational amplifier to the supply voltage</i>	147
6.3.7	<i>A monostable multivibrator based on an operational amplifier</i>	148
6.3.8	<i>Voltage stabilization based on an operational amplifier</i>	149
6.3.9	<i>Voltage stabilization based on a Darlington pair and an operational amplifier</i>	150
6.3.10	<i>Questions</i>	152
6.3.11	<i>Further investigation</i>	153
6.4	<i>Voltage-to-frequency converters which make use of an operational amplifier</i>	153
6.4.1	<i>A voltage-to-frequency converter based on a unijunction transistor</i>	153
6.4.2	<i>A voltage-to-frequency converter based on a programmable unijunction transistor</i>	155
6.4.3	<i>A voltage-to-frequency converter based on a free-running multivibrator utilizing field-effect transistors</i>	155
6.5	<i>A high-quality pre-amplifier for audio-frequency signals</i>	156
6.5.1	<i>The frequency response of the audio-frequency amplifier</i>	159

## CONTENTS

6.5.2	<i>The dependence of the amplifier voltage gain on the supply voltage</i>	160
6.5.3	<i>The dependence of the amplifier performance on the characteristics of the individual transistor</i>	160
6.5.4	<i>An equalization network</i>	161
6.5.5	<i>Further Investigations</i>	163
6.5.6	<i>The input impedance of the pre-amplifier</i>	163
7	<b>Logic Gates</b>	
7.1	<b>Introduction</b>	164
7.1.1	<i>TTL and CMOS compared</i>	164
7.1.2	<i>Basic constraints on TTL circuit design and operation</i>	165
7.1.3	<i>A logic probe</i>	166
7.2	<b>The basic TTL 2-input NAND gate</b>	169
7.2.1	<i>The SN7400N quad 2-input NAND unit</i>	170
7.3	<b>Multivibrator circuits based on NAND gates of the TTL type</b>	171
7.3.1	<i>A bistable circuit based on the use of two 2-input NAND gates</i>	172
7.4	<b>Further pulse generator circuits based on NAND gates</b>	173
7.5	<b>The OR and the exclusive-OR functions</b>	174
7.6	<b>Complementary metal-oxide semiconductor (CMOS) logic gates</b>	175
7.6.1	<i>A NAND gate</i>	176
7.6.2	<i>The power consumption of a CMOS gate</i>	177
7.6.3	<i>The current flow to a CMOS gate in the ambient and switching modes</i>	177
7.6.4	<i>The power consumption of a TTL gate</i>	178
7.6.5	<i>Rise time, fall time and propagation time for a CMOS gate</i>	179
7.6.6	<i>Further investigations</i>	181
7.7	<b>Multivibrator circuits based on NAND gates of the CMOS type</b>	181
8	<b>Some integrated Circuits</b>	
8.1	<b>Introduction</b>	183
8.1.1	<i>An integrated circuit electronic timer</i>	184
8.1.2	<i>Monostable or 'one-shot' operation of the electronic timer</i>	186
8.1.3	<i>Astable (free-running) operation of the electronic timer</i>	188
8.1.4	<i>Use of the electronic timer (555) to provide a linear voltage ramp</i>	189
8.1.5	<i>Effect of the control voltage on the monostable operation of the electronic timer 555.</i>	190

8.1.6	<i>Further investigation</i>	191
8.2	<b>A monolithic integrated circuit voltage stabilizer</b>	192
8.2.1	<i>To determine the voltage stabilization factor <math>S_V</math> of the ic voltage regulator</i>	192
8.3	<b>Voltage-to-frequency converters</b>	194
8.3.1	<i>A voltage-to-frequency converter based on two operational amplifiers in an integrated circuit module</i>	195
8.3.2	<i>An alternative voltage-to-frequency converter based on the 747 dual opamp ic</i>	197
8.4	<b>Monolithic integrated circuit waveform generators</b>	198
8.4.1	<i>The power supply connections of the ic waveform generator</i>	201
8.4.2	<i>The use of external timing components with the ic waveform generator</i>	203
8.4.3	<i>Independence of the frequency of the supply voltage of the ic waveform generator</i>	204
8.4.4	<i>Sine-wave distortion of the ic waveform generator</i>	204
8.4.5	<i>The ic waveform generator as a voltage-controlled oscillator</i>	205
8.5	<b>Waveform generators of the multivibrator type based on NAND gates</b>	206
8.5.1	<i>Astable (free-running) multivibrators based on (a) a SN 7400N and (b) a CMOS unit 4011</i>	206
8.5.2	<i>An ic monostable multivibrator</i>	210
8.5.3	<i>A Schmitt trigger circuit based on two 2-input NAND gates</i>	210
8.5.4	<i>Additional investigation</i>	212
8.6	<b>A decade counter and a cold-cathode number display tube</b>	212
8.6.1	<i>Shaping the input pulses</i>	216
8.6.2	<i>Dialling-in decimal numbers to be added</i>	217
8.6.3	<i>The decadecounter and its BCD output</i>	218
8.6.4	<i>Counting the pulses from a low-frequency frequency multivibrator</i>	219
	<b>Appendix</b>	220
	<b>Index</b>	223