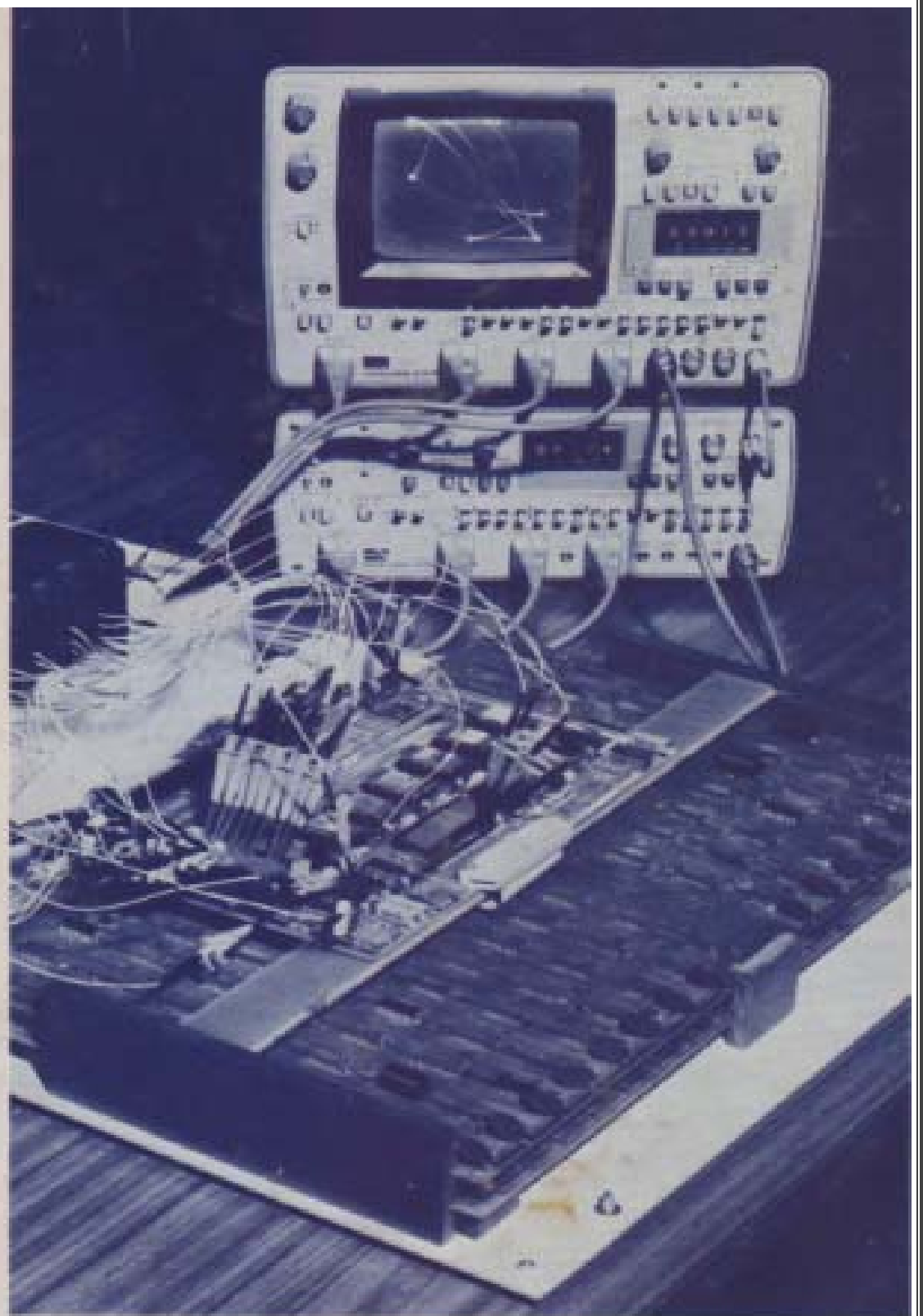




ELECTRONIC MEASUREMENTS

Kantrowitz / Kousourou / Zucker



CONTENTS

PREFACE	<i>xi</i>
----------------	-----------

1

MEASUREMENT PARAMETERS *1*

1.1	Introduction	<i>1</i>
1.2	Measurement Process	<i>2</i>
1.3	Fundamental Units	<i>2</i>
1.4	Systems of Units	<i>2</i>
1.5	Derived Units	<i>4</i>
1.6	Multiples and Divisions of Units	<i>5</i>
1.7	Unit Conversions	<i>5</i>
1.8	Standards	<i>6</i>
1.9	Errors	<i>7</i>
1.10	Accuracy	<i>7</i>
1.11	Precision	<i>8</i>
1.12	Range	<i>8</i>
1.13	Span	<i>8</i>
1.14	Sensitivity	<i>9</i>
1.15	Loading Effect	<i>9</i>
1.16	Summary	<i>9</i>
	Review Questions	<i>10</i>

2**DIRECT CURRENT, VOLTAGE,
AND RESISTANCE MEASUREMENTS 11**

2.1	Introduction	11
2.2	Galvanometer	11
2.3	dc Ammeters	18
2.4	dc Voltmeters	23
2.5	Ohmmeters and Resistance Measurements	27
2.6	Ammeter-voltmeter Method	28
2.7	Series Ohmmeter	29
2.8	Shunt Ohmmeter	30
2.9	Voltage Divider Ohmmeter	31
2.10	Megger®	32
2.11	Wheatstone Bridge Method	35
2.12	Kelvin Bridge Method	38
2.13	Multimeters (VOM)	40
2.14	Electronic Multimeter (EMM)	42
2.15	Analog Multimeter	44
2.16	Digital Multimeters	47
2.17	Summary	51
	Review Questions	51

3**ALTERNATING CURRENT MEASUREMENTS 52**

3.1	Introduction	52
3.2	Sine Wave	52
3.3	Frequency Response	54
3.4	Meters and the Measurement	55
3.5	Electrodynamometer Movement	56
3.6	Iron Vane Meter Movement	57
3.7	Rectifying ac for Measurement	59
3.8	Rectifier-type Meters	61
3.9	Direct rms Responding Instruments	62
3.10	Peak Responding Voltmeters	67
3.11	Meter Specifications	70
3.12	Current Measurements	71
3.13	Summary	73
	Review Questions	74

4**POWER MEASUREMENTS 75**

- 4.1 Power Defined 75
- 4.2 Three Types of ac Power 76
- 4.3 Power Factor Correction 78
- 4.4 Electrodynamometer Wattmeter 79
- 4.5 Compensated Wattmeters 80
- 4.6 Measurement of Power in Three-phase Circuits 81
- 4.7 Three Wattmeter Method 82
- 4.8 Two Wattmeter Method 85
- 4.9 Wattmeter Specifications 86
- 4.10 Reactive Power Measurements 88
- 4.11 Power-factor Meter 89
- 4.12 Watt-hour Meter 90
- 4.13 Power Measurement at Higher Frequencies 93
- 4.14 Calorimeter Power Meter 94
- 4.15 Bolometer 96
- 4.16 Summary 99
- Review Questions 99

5**OSCILLOSCOPE MEASUREMENTS 102**

- 5.1 Introduction 102
- 5.2 Basic Oscilloscope Operation 103
- 5.3 Simplified Functional Block of an Oscilloscope 107
- 5.4 Vertical Amplifier Attenuator 107
- 5.5 Sweep Synchronization Circuit 107
- 5.6 Sweep Generator—Horizontal Amplifier 109
- 5.7 Dual Trace Scope Feature 112
- 5.8 Sweep Magnification Feature 114
- 5.9 Delayed Sweep Feature 115
- 5.10 Sampling Oscilloscope 117
- 5.11 Oscilloscope Probes 117
- 5.12 Vertical Amplifier Calibration
and Attenuator Compensation 120
- 5.13 Voltage Measurements 121
- 5.14 Frequency Measurements 123
- 5.15 Phase Measurements 126

5.16	Current Measurements	129
5.17	Power Measurements	129
5.18	Square-wave Testing	129
5.19	Pulse Measurements	133
5.20	Receiver Alignment	136
5.21	Summary	136
	Review Questions	137

6

DISCRETE COMPONENT MEASUREMENTS 139

6.1	Introduction	139
6.2	Impedance Concepts	139
6.3	Resistance Measurement (Low Frequency)	144
6.4	ac Impedance Measurements (Line Frequency Power) Via Ammeter-voltmeter-wattmeter Method	146
6.5	Low-Frequency ac Capacitor Measurements	147
6.6	Inductance Bridge Measurements	151
6.7	Impedance Bridges	153
6.8	High-frequency Component Measurements Utilizing the Q Meter	154
6.9	Summary	159
	Review Questions	164

7

BASIC SEMICONDUCTOR MEASUREMENTS 165

7.1	Introduction	165
7.2	Diode (Rectifier) Measurements	165
7.3	Measurement of Zener Diodes	171
7.4	Silicon Control Rectifier (SCR) Measurements— Theory of Operation	173
7.5	Transistor Measurements	176
7.6	Field-effect Transistor	183
7.7	Semiconductor Test Instruments	190
7.8	Summary	192
	Review Questions	193

8**INTEGRATED CIRCUIT MEASUREMENTS 195**

- 8.1 Introduction 195
- 8.2 Operational Amplifier—Theory of Operation 196
- 8.3 Operational Amplifier Characteristics and Measurements 199
- 8.4 Digital Integrated Circuits 214
- 8.5 Transistor-Transistor Logic (TTL) Integrated Circuit 214
- 8.6 Measurement of TTL SN 54/74 NAND Gate
Characteristics 219
- 8.7 Summary 224
- Review Questions 225

9**HIGH-FIDELITY AUDIO
SYSTEMS AND TESTING 227**

- 9.1 Introduction 227
- 9.2 High-fidelity Systems—Conceptual Remarks 227
- 9.3 Distortion Concepts and Measurements 228
- 9.4 Spectrum Analyzers 245
- 9.5 Other Audio Frequency Measuring Instruments 256
- 9.6 Ratings of Audio Electronic Devices 257
- 9.7 Summary 258
- Review Questions 259

10**RECORDERS AND RECORDING SYSTEMS 261**

- 10.1 Chart Recorders—Conceptual Remarks 261
- 10.2 Recording Systems Measurements 279
- 10.3 Summary 289
- Review Questions 290

11**TRANSDUCER SYSTEMS 292**

- 11.1 Introduction 292
- 11.2 Principles of Transducers and Measurements 294

11.3	Sound Measurements	313
11.4	Sound Transducers	314
11.5	The Miniature (Ceramic) Electret Microphone	315
11.6	Vibration Transducers	315
11.7	Mechanical Impedance Measurements	316
11.8	High-frequency Loudspeaker Transducer	316
11.9	No-touch Sensors	317
11.10	Summary	317
	Review Questions	319

12

SIGNAL GENERATION: APPLICATIONS AND MEASUREMENTS 321

12.1	Introduction	321
12.2	Function Generators	321
12.3	Oscillators	322
12.4	Pulse and Square-wave Generators	326
12.5	Basic Electronic Counter Principles	336
12.6	Summary	345
	Review Questions	346

13

RADIO AND MICROWAVE FREQUENCY SYSTEMS 347

13.1	Introduction	347
13.2	Radio Frequency Spectrum Analyzers	348
13.3	Modulation Measurements	350
13.4	Intermodulation (Third-Order Intercept) Distortion	355
13.5	Visual Alignment Signal Generators for Radio Receivers	355
13.6	Microwave Measuring Devices	359
13.7	Summary	364
13.8	Appendix	367
	Review Questions	373

Appendix

GLOSSARY OF INSTRUMENT TERMS 375

DBM TO VOLTAGE CONVERSION 389

INDEX 391