

The diagram illustrates radiation shielding and grounding techniques. It features a central circular source emitting radiation, represented by concentric circles and arcs. The radiation is shown being blocked by a horizontal barrier with diagonal hatching. Below the barrier, the radiation is reflected back up, indicated by upward-pointing arrows and arcs. The top part of the diagram shows the radiation being directed downwards towards the barrier, with arrows pointing to the barrier's surface.

**Grounding and  
Shielding Techniques**  
*Fourth Edition*

Ralph Morrison

# CONTENTS

---

Preface

xi

## 1 Electrostatics

1

- 1.1 Introduction, 1
- 1.2 The Low-Frequency Signal Definition, 3
- 1.3 Charge, 4
- 1.4 Forces Between Charges, 4
- 1.5 Electric Field, 5
- 1.6 The  $E$  Field for Charge Distributions, 6
- 1.7 The Concept of Voltage, 6
- 1.8 Voltage Gradient, 7
- 1.9 Spherical Conductor with a Charge, 8
- 1.10 Capacitance, 9
- 1.11 The Displacement Field  $D$ , 9
- 1.12 Field Representations, 10
- 1.13 Points of Difficulty, 12
- 1.14 MKS System of Units, 12
- 1.15 Charges on Spherical Shells, 14
- 1.16 The Earth Plane, 15
- 1.17 Typical Charge Distributions, 16
- 1.18 Cylindrical Surfaces, 17
- 1.19 Parallel Plate Capacitors, 19
- 1.20 Electric Field Energy, 20
- 1.21 Self- and Mutual Capacitance, 21
- 1.22 Example of Mutual Capacitance, 22

- 1.23 Importance of Electric Field Concepts, 22
- 1.24 A Powerful Tool, 23

## 2 Magnetics

25

- 2.1 Introduction, 25
- 2.2 Lines of Force and Flux, 26
- 2.3 The  $B$  Field, 26
- 2.4 The  $H$  Field, 27
- 2.5 Faraday's Law, 29
- 2.6 The Magnetic Circuit, 29
- 2.7 The Transformer, 31
- 2.8 Hysteresis—Magnetic Materials, 33
- 2.9 Inductance, 35
- 2.10 The Inductance of a Solenoid, 35
- 2.11 Energy in the Magnetic Field, 36
- 2.12 Magnetic Units, 36
- 2.13 Leakage Inductance, 37
- 2.14 The Audio Transformer, 39
- 2.15 Magnetic Storms, 39
- 2.16 Spacecraft Potentials, 40
- 2.17 The  $E$  and  $H$  Fields Together, 40
- 2.18 Fields and Components, 41
- 2.19 The Inductance of Isolated Conductors, 42

## 3 The Transport of Signals and Power

43

- 3.1 Introduction, 43
- 3.2 The Transmission Line, 44
- 3.3 Transmission Line Terminations, 45
- 3.4 Transmission Line Fields, 47
- 3.5 Ground Planes, 49
- 3.6 Coaxial Transmission Lines, 50
- 3.7 Sine Waves and Transmission Lines, 50
- 3.8 Terminations, 53
- 3.9 Poynting's Vector, 54
- 3.10 Radiation, 55
- 3.11 Radiation from a Dipole, 56
- 3.12 Radiation from a Current Loop, 57
- 3.13 Effective Radiating Power, 59

**4 Fields and Conductors**

61

- 4.1 Introduction, 61
- 4.2 Ohms per Square, 62
- 4.3 Reflection, 64
- 4.4 Skin Effect, 64
- 4.5 Shielding Effectivity, 65
- 4.6 Apertures, 66
- 4.7 Independent and Dependent Apertures, 67
- 4.8 Closing Apertures, 67
- 4.9 Waveguides Beyond Cutoff, 68
- 4.10 A Review of Fields Entering an Enclosure, 69
- 4.11 The Coupling of Fields to Circuits, 69
- 4.12 The Fields in a Room, 71
- 4.13 Common Mode and Normal Mode, 73

**5 Electrostatic Shielding—I**

75

- 5.1 Introduction, 75
- 5.2 The Circuit in a "Box", 76
- 5.3 External Grounding of One Conductor, 78
- 5.4 The Game, 78
- 5.5 The Transformer Connection, 81
- 5.6 The Single Transformer Shield, 82
- 5.7 The Three-Shield Solution, 84
- 5.8 The Single-Ended Instrument, 85
- 5.9 Single-Ended Signal Sources, 86
- 5.10 Balanced Signal Sources, 87
- 5.11 The Two-Ground Problem, 88
- 5.12 The Fundamental Instrumentation Problem, 90
- 5.13 The Differential Amplifier, 91

**6 Electrostatic Shielding—II**

93

- 6.1 Shielding Low-Frequency Signals, 93
- 6.2 Shielding Single-Ended Signals, 94
- 6.3 Shielding Balanced Sources, 96
- 6.4 Floating Circuits, 97
- 6.5 Shielding Grounded Unbalanced Circuits, 98
- 6.6 Shielding Electronic Equipment, 99
- 6.7 Shielding Instrumentation Amplifiers, 100

- 6.8 The Driven Shield, 103
- 6.9 The Analog Input Cable, 104
- 6.10 Aluminum Foil Shielding, 105
- 6.11 The Drain Wire, 105
- 6.12 Low-Noise Cable, 106
- 6.13 Reactive Coupling in Circuits, 107
- 6.14 Guard Rings, 108

## **7 Common-Impedance Coupling** 111

- 7.1 Introduction, 111
- 7.2 Amplifier Common Impedance, 112
- 7.3 Strain-Gage Excitation Supplies, 112
- 7.4 Transformer Shielding for Excitation Supplies, 116
- 7.5 Star Connections, 117
- 7.6 Neutrals as Common Impedances, 119
- 7.7 The Earth as a Common Impedance, 120
- 7.8 The Forward Referencing Amplifier, 122
- 7.9 Driven Power Stages (Isolated Output), 123

## **8 Circuit Designs** 127

- 8.1 Introduction, 127
- 8.2 Common-Mode Rejection—Postmodulation, 128
- 8.3 The Common-Mode Attenuator, 128
- 8.4 High-Input Impedance Circuits, 130
- 8.5 Balanced Excitation Supplies, 133
- 8.6 Charge Amplifiers, 134
- 8.7 Charge Amplifiers and Calibration, 137
- 8.8 Calibration Guarding, 137
- 8.9 Filtering Analog Signals, 138
- 8.10 The ac Amplifier, 140
- 8.11 Suppression Circuits, 140
- 8.12 Switching Regulators, 142
- 8.13 Off-Line Switchers, 144
- 8.14 Mounting Switching Transistors or FETs, 144
- 8.15 Parallel Active Components, 145
- 8.16 The Medical Problem, 145
- 8.17 The Mad Cow Problem, 148

**9 Utility Power**

149

- 9.1 Introduction, 149
- 9.2 The Ground Plane, 150
- 9.3 Single-Point Grounding of Ground Planes, 151
- 9.4 Racks as a Ground Plane, 152
- 9.5 Extensions of a Ground Plane, 153
- 9.6 The Earth as a Ground Plane, 153
- 9.7 Isolated Grounds, 154
- 9.8 Separately Derived Power, 155
- 9.9 Power Isolation Transformers, 156
- 9.10 Computer Power Centers, 157
- 9.11 Power-Line Filters, 158
- 9.12 Facility Power Filters, 159
- 9.13 Transient Power Loads, 160
- 9.14 Controllers, 161
- 9.15 Transient Protection, 162
- 9.16 Ungrounded Power, 163
- 9.17 The NEC and Power Connections, 163
- 9.18 Bending Magnetic Fields, 164

**10 High-Frequency Design**

167

- 10.1 Introduction, 167
- 10.2 The PC Board, 168
- 10.3 PC Ground Planes, 169
- 10.4 PC Board Transmission Lines, 169
- 10.5 PC Boards and Radiation, 170
- 10.6 PC Boards Decoupling Capacitors, 170
- 10.7 PC Boards—Ground Planes and Power Planes, 171
- 10.8 PC Boards—Ribbon Cable, 172
- 10.9 High-Frequency Transport and Open Cable, 173
- 10.10 High-Frequency Transport Over Coax, 174
- 10.11 Cable Transfer Impedance, 174
- 10.12 Cable Shield Terminations, 175
- 10.13 The Chattering Relay Test, 177
- 10.14 The Bond, 178
- 10.15 The Transport of High-Frequency Power, 179
- 10.16 Mixing Analog and Digital Signals, 179
- 10.17 The Sniffer, 179
- 10.18 Screen Rooms, 180
- 10.19 Screen Room Power Filters, 181

- 10.20 Grounding the Screen Room, 181
- 10.21 The Screen Room Design, 182
- 10.22 Using a Screen Room, 182

## **11 Pulses and Step Functions** **185**

- 11.1 Introduction, 185
- 11.2 Spectrum of a Square Wave, 186
- 11.3 Spectrum of a Single Event, 188
- 11.4 A Valuable Calculating Tool, 191
- 11.5 The ESD (Electrostatic Discharge), 191
- 11.6 ESD Protection, 192
- 11.7 ESD and Its Characteristics, 192
- 11.8 ESD Testing, 193

## **Index** **195**